# Design of the Folded Cascode OTA

Version 1

Christian Enz

2025 - 05 - 22

# **Table of contents**

1	Introduction	3
2	Analysis         2.1 Small-signal analysis	. 4
	2.2.1 Input-referred thermal noise	
	2.2.2 Input-referred flicker noise	
3	Design	8
•	3.1 Specifications	
	3.2 Process	
	3.3 Design procedure	
	3.3.1 Sizing the differential pair $M_{1a}$ - $M_{1b}$	
	3.4 Sizing of $M_{3a}$ - $M_{3b}$	
	3.5 Sizing of $M_{4a}$ - $M_{4b}$ and $M_{5a}$ - $M_{5b}$	
	3.6 Sizing of $M_{2a}$ - $M_{2b}$ - $M_{2c}$	
	0 20 20 20	
	3.7 Sizing $M_{7a}$ - $M_{7b}$	
	9 1- 1-	
	v	
	3.9.1 Specifications	
	3.9.2 Bias	
	3.9.3 Transistor information	. 16
4	OTA Characteristics	18
•	4.1 Open-loop gain	_
	4.2 Input-referred noise	
	4.3 Input-referred offset	
	4.4 Current and power consumption	
	4.4 Current and power consumption	. 21
5	Simulation results from ngspice	23
	5.1 Operating point	. 23
	5.2 Large-signal differential transfer characteristic	
	5.3 Open-loop gain	
	5.4 Input-referred noise	
	5.5 Input common-mode voltage range	
	5.6 Step-response	
	5.6.1 Small-step	
	5.6.2 Large step	
	5.7 Current and power consumption	
		. 55
6	Conclusion	34
Re	ferences	35

## 1 Introduction

 


Figure 1.1: Schematic of the folded cascode differential OTA [1].

#### Note

Note that all nMOS transistors in Figure 1.1 have an odd number and all the pMOS transistors an even number which explains the numbering process (this is the reason why there is no  $M_6$  transistor!).

This notebook presents the design of the folded cascode differential OTA [1] shown in Figure 1.1 for the same specifications used for the other OTAs. The folded cascode OTA is similar to the telescopic OTA except that the current  $I_{b3}$  flowing in the current mirror  $M_{3a}$ - $M_{3b}$  can be different than the current  $I_{b1}$  flowing in the differential pair. How to choose the ratio  $\alpha \triangleq I_{b3}/I_{b1}$ ? If the current  $I_{b3}$  is made equal to current  $I_{b1}$  ( $\alpha = 1$ ), then if the differential input voltage is largely positive, the differential pair will saturate and all the bias current  $2I_{b1}$  is then steered into  $M_{1a}$ . This means that all the bias current  $I_{b2}$  is flowing into  $M_{1a}$  and no current is available at the input of the cascode current mirror  $M_{3a}$ - $M_{3b}$ . This situation should be avoided because it introduces an additional delay to charge the parasitic capacitance at node 3 and bring the current mirror  $M_{3a}$ - $M_{3b}$  back to normal operation. Usually, the ratio  $\alpha$  is taken  $1.2 < \alpha < 2$ . In order to minimize the current consumption, we will choose  $\alpha = 1.2$ . This means that the folded cascode OTA unavoidably consumes more current than the telescopic OTA (more than twice).

We will start with a detailed analysis of the OTA which will allow to derive all the design equations that will be used in the design phase. The OTA is then designed for a given set of specifications for the chosen IHP SG13G2 130nm BiCMOS technology [2]. We have selected this technology because IHP provides an open source PDK which is then used for the validation of the design by simulation with ngspice [3] using the PSP compact model [4] provided by the open source PDK [2].

## 2 Analysis

### 2.1 Small-signal analysis

In a 1<sup>st</sup>-order analysis, we can neglect the capacitances at the low impedance cascode nodes 4, 5, 6 and 7 and only account for the capacitances at high impedance nodes 3 (gate of current mirror  $M_{3a}$ - $M_{3b}$ ) and out (output node). The circuit becomes similar to that of the simple OTA, with the dominant pole  $\omega_0$  at the output node (out) and the non-dominant pole  $\omega_p$  at the current mirror node 3. The transfer function also has a pole-zero doublet. Its transfer function is then given by

$$A_{dm}(s) \triangleq \frac{\Delta V_{out}}{\Delta V_{in}} \cong A_{dc} \cdot \frac{1 + s/\omega_z}{(1 + s/\omega_0)(1 + s/\omega_p)} \cong \frac{A_{dc}}{1 + s/\omega_0} \cong \frac{\omega_u}{s}, \tag{2.1}$$

where

$$A_{dc} \cong \frac{G_{m1}}{G_o},\tag{2.2}$$

$$G_o \cong \frac{G_{ds3} G_{ds5}}{G_{ms5}} + \frac{(G_{ds1} + G_{ds2}) G_{ds4}}{G_{ms4}},$$
 (2.3)

$$\omega_0 \cong \frac{G_o}{C_L},\tag{2.4}$$

$$\omega_p \cong \frac{G_{m3}}{C_3},\tag{2.5}$$

$$\omega_z = 2\,\omega_p,\tag{2.6}$$

$$\omega_u = A_{dc} \cdot \omega_0 \cong \frac{G_{m1}}{C_L}. \tag{2.7}$$

## 2.2 Noise Analysis

At low-frequency the noise of the cascode transistors  $M_{4a}$ - $M_{4b}$  and  $M_{5a}$ - $M_{5b}$  can be neglected and the noise analysis is then identical to that of the simple OTA. The PSD of the output noise current is given by

$$S_{nout} \cong 2\left(S_{I_{n1}} + S_{I_{n2}} + S_{I_{n3}}\right) \tag{2.8}$$

which can be expressed in terms of the output noise conductance

$$S_{nout} = 4kT \cdot G_{nout}, \tag{2.9}$$

where

$$G_{nout} \cong 2 (G_{n1} + G_{n2}G_{n3}),$$
 (2.10)

with

$$G_{ni} = \gamma_{ni} \cdot G_{mi} + G_{mi}^2 \cdot \frac{\rho_i}{W_i L_i f}$$
 for  $i = 1, 2, 3$ . (2.11)

The input-referred noise resistance is then given by

$$R_{nin} \triangleq \frac{G_{nout}}{G_{m1}^2} = \frac{2(G_{n1} + G_{n2} + G_{n3})}{G_{m1}^2} = \frac{2G_{n1}}{G_{m1}^2} \cdot \left(1 + \frac{G_{n2}}{G_{n1}} + \frac{G_{n3}}{G_{n1}}\right)$$
(2.12)

which we rewrite as

$$R_{nin} = \frac{2G_{n1}}{G_{m1}^2} \cdot (1+\eta) \tag{2.13}$$

with

$$\eta = \frac{G_{n2}}{G_{n1}} + \frac{G_{n3}}{G_{n1}}. (2.14)$$

 $\eta$  represents the contribution of the current source  $M_{2b}$ - $M_{2c}$  and the current mirror  $M_{3a}$ - $M_{3b}$  referred to the input and normalized to the contribution of the differential pair  $M_{1a}$ - $M_{1b}$ . Of course during the design phase we will try to minimize  $\eta$ .

#### 2.2.1 Input-referred thermal noise

The input-referred thermal noise resistance is given by

$$R_{nth} = \frac{2\gamma_{n1}}{G_{m1}} \cdot (1 + \eta_{th}), \tag{2.15}$$

where

$$\eta_{th} = \frac{\gamma_{n2}}{\gamma_{n1}} \cdot \frac{G_{m2}}{G_{m1}} + \frac{\gamma_{n3}}{\gamma_{n1}} \cdot \frac{G_{m3}}{G_{m1}} \tag{2.16}$$

represents the contribution to the input-referred thermal noise of the current source  $M_{2b}$ - $M_{2c}$  and the current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair  $M_{1a}$ - $M_{1b}$ . In case  $G_{m1} \gg G_{m2}$  and  $G_{m1} \gg G_{m3}$ , then  $\eta_{th} \ll 1$  and the thermal noise is dominated by the input differential pair. Eqn. (2.15) can then be simplified to

$$R_{nth} \cong \frac{2\gamma_{n1}}{G_{m1}}. (2.17)$$

The OTA thermal noise excess factor is defined as

$$\gamma_{ota} \triangleq G_m \cdot R_{nth} \tag{2.18}$$

with  $G_m = G_{m1}$  the OTA equivalent transconductance. The OTA thermal noise excess factor then writes

$$\gamma_{ota} = 2\gamma_{n1} \cdot (1 + \eta_{th}). \tag{2.19}$$

In the case  $G_{m1} \gg G_{m2}$  and  $G_{m1} \gg G_{m3}$ , then  $\eta_{th} \ll 1$  and the noise is dominated by the input differential pair  $M_{1a}$ - $M_{1b}$ . The OTA thermal noise excess factor can then be simplified as

$$\gamma_{ota} \cong 2 \gamma_{n1}. \tag{2.20}$$

#### 2.2.2 Input-referred flicker noise

The input-referred flicker noise is given by

$$R_{nfl} = \frac{2}{f} \left[ \frac{\rho_n}{W_1 L_1} + \left( \frac{G_{m2}}{G_{m1}} \right)^2 \frac{\rho_p}{W_2 L_2} + \left( \frac{G_{m3}}{G_{m1}} \right)^2 \frac{\rho_n}{W_3 L_3} \right]$$
(2.21)

which can be rewritten as

$$R_{nfl} = \frac{2\rho_n}{W_1 L_1 f} \cdot (1 + \eta_{fl}) \tag{2.22}$$

where

$$\eta_{fl} = \frac{\rho_p}{\rho_n} \left(\frac{G_{m2}}{G_{m1}}\right)^2 \frac{W_1 L_1}{W_2 L_2} + \left(\frac{G_{m3}}{G_{m1}}\right)^2 \frac{W_1 L_1}{W_3 L_3}$$
(2.23)

represents the contribution to the input-referred flicker noise of the current source  $M_{2b}$ - $M_{2c}$  and the current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair  $M_{1a}$ - $M_{1b}$ .

The corner frequency is the frequency at which the flicker noise becomes equal to the thermal noise

$$R_{nfl}(f = f_k) = R_{nth} \tag{2.24}$$

which is given by

$$f_k = \frac{1}{R_{nth}} \cdot \frac{2\rho_n}{W_1 L_1} \cdot (1 + \eta_{fl}) = \frac{G_{m1} \rho_n}{\gamma_{n1} W_1 L_1} \cdot \frac{1 + \eta_{fl}}{1 + \eta_{th}}.$$
 (2.25)

The transconductance  $G_{m1}$  is set by the constraints either on thermal noise or on bandwidth (GBW product). The corner frequency  $f_k$  can be reduced by increasing  $W_1 L_1$  but also  $W_2 L_2$  and  $W_3 L_3$  at the same time to conserve the same  $\eta_{fl}$  factor. Assuming that  $G_{m2}/G_{m1} \ll 1$  and  $G_{m1} \gg G_{m3}$ , as required by the constraints on minimizing the contribution of the current source  $M_{2b}-M_{2c}$  and current mirror  $M_{3a}-M_{3b}$  to the input-referred offset and thermal noise, then  $\eta_{th} \ll 1$  and  $\eta_{fl} \ll 1$  and the corner frequency  $f_k$  is then mainly set by the differential pair transconductance and gate transistor area

$$f_k \cong \frac{G_{m1} \,\rho_n}{\gamma_{n1} \,W_1 \,L_1}.\tag{2.26}$$

## 2.3 Input-referred offset voltage

The offset analysis is similar to that of the simple OTA because the contribution of the mismatch of the cascode transistors can be neglected. The random offset current is then mainly due to the mismatch between  $M_{1a}$  and  $M_{1b}$ ,  $M_{2b}$  and  $M_{2c}$  and  $M_{3a}$  and  $M_{3b}$ . The variance of the output offset current is then given by

$$\sigma_{I_{os}}^2 \cong \sigma_{\Delta I_{D1}}^2 + \sigma_{\Delta I_{D2}}^2 + \sigma_{\Delta I_{D3}}^2 = I_{b1}^2 \cdot \sigma_{\frac{\Delta I_{D1}}{I_{D1}}}^2 + I_{b2}^2 \cdot \sigma_{\frac{\Delta I_{D2}}{I_{D2}}}^2 + I_{b3}^2 \cdot \sigma_{\frac{\Delta I_{D3}}{I_{D3}}}^2, \tag{2.27}$$

with

$$\sigma_{\frac{\Delta I_{Di}}{I_{Di}}}^2 = \sigma_{\beta_i}^2 + \left(\frac{G_{mi}}{I_b}\right)^2 \sigma_{V_{Ti}}^2 \quad \text{for } i = 1, 2, 3,$$
(2.28)

where

$$\sigma_{\beta_i}^2 = \frac{A_{\beta}^2}{W_i L_i}$$
 for  $i = 1, 2, 3$  (2.29)

are the  $\beta$ -mismatches and

$$\sigma_{V_{T_i}}^2 = \frac{A_{V_T}^2}{W_i L_i}$$
 for  $i = 1, 2, 3$  (2.30)

are the  $V_T$ -mismatches.

The variance of the output offset current then becomes

$$\sigma_{I_{os}}^2 = I_{b1}^2 \cdot \sigma_{\beta_1}^2 + I_{b2}^2 \cdot \sigma_{\beta_2}^2 + I_{b3}^2 \cdot \sigma_{\beta_3}^2 + G_{m1}^2 \cdot \sigma_{V_{T1}}^2 + G_{m2}^2 \cdot \sigma_{V_{T2}}^2 + G_{m3}^2 \cdot \sigma_{V_{T3}}^2. \tag{2.31}$$

The variance of the input-referred offset voltage is obtained by dividing the variance of the output offset current by  $G_{m1}^2$  resulting in

$$\sigma_{V_{os}}^2 = \sigma_{V_T}^2 + \sigma_{\beta}^2. \tag{2.32}$$

 $\sigma_{V_T}^2$  is the  $V_T$ -mismatch given by

$$\sigma_{V_T}^2 = \sigma_{V_{T1}}^2 \cdot (1 + \xi_{V_T}) \tag{2.33}$$

where

$$\xi_{V_T} = \left(\frac{G_{m2}}{G_{m1}}\right)^2 \cdot \frac{\sigma_{V_{T2}}^2}{\sigma_{V_{T1}}^2} + \left(\frac{G_{m3}}{G_{m1}}\right)^2 \cdot \frac{\sigma_{V_{T3}}^2}{\sigma_{V_{T1}}^2} \tag{2.34}$$

represents the  $V_T$ -mismatch contributions to the input-referred offset of the current source  $M_{2b}$ - $M_{2c}$  and current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair with

$$\sigma_{V_{T1}} = \frac{A_{V_{Tn}}^2}{W_1 L_1},\tag{2.35}$$

$$\sigma_{V_{T2}} = \frac{A_{V_{Tp}}^2}{W_2 L_2},\tag{2.36}$$

$$\sigma_{V_{T3}} = \frac{A_{V_{Tn}}^2}{W_3 L_3},\tag{2.37}$$

 $\sigma_{\beta}^2$  is the  $\beta$ -mismatch given by

$$\sigma_{\beta}^2 = \left(\frac{I_{b1}}{G_{m1}}\right)^2 \cdot \sigma_{\beta_1}^2 \cdot (1 + \xi_{\beta}) \tag{2.38}$$

where

$$\xi_{\beta} = \left(\frac{I_{b2}}{I_{b1}}\right)^2 \frac{\sigma_{\beta_2}^2}{\sigma_{\beta_1}^2} + \left(\frac{I_{b3}}{I_{b1}}\right)^2 \frac{\sigma_{\beta_3}^2}{\sigma_{\beta_1}^2} \tag{2.39}$$

represents the  $\beta$ -mismatch contributions to the input-referred offset of the current source  $M_{2b}$ - $M_{2c}$  and current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair with

$$\sigma_{\beta_1}^2 = \frac{A_{\beta_n}^2}{W_1 L_1},\tag{2.40}$$

$$\sigma_{\beta_2}^2 = \frac{A_{\beta_p}^2}{W_2 L_2},\tag{2.41}$$

$$\sigma_{\beta_3}^2 = \frac{A_{\beta_n}^2}{W_3 L_3}. (2.42)$$

Replacing in (2.34) and (2.39) results in

$$\xi_{V_T} = \left(\frac{G_{m2}}{G_{m1}}\right)^2 \left(\frac{A_{V_{Tp}}}{A_{V_{Tp}}}\right)^2 \frac{W_1 L_1}{W_2 L_2} + \left(\frac{G_{m3}}{G_{m1}}\right)^2 \frac{W_1 L_1}{W_3 L_3}$$
(2.43)

and

$$\xi_{\beta} = \left(\frac{I_{b2}}{I_{b1}}\right)^2 \left(\frac{A_{\beta_p}}{A_{\beta_n}}\right)^2 \frac{W_1 L_1}{W_2 L_2} + \left(\frac{I_{b3}}{I_{b1}}\right)^2 \frac{W_1 L_1}{W_2 L_2}.$$
 (2.44)

Similarly to the flicker noise, the input-referred offset (variance or standard deviation) can be reduced by increasing the area  $W_1 L_1$  of  $M_{1a}$ - $M_{1b}$  but at the same time also increasing the area  $W_2 L_2$  of the current source  $M_{2b}$ - $M_{2c}$  and also the area  $W_3 L_3$  of the current mirror  $M_{3a}$ - $M_{3b}$ .

## Design

### 3.1 Specifications

The OTA specifications are given in Table 3.1.



#### Warning

An important limitation of the IHP SC13G2 BiCMOS technology [2] is the high output conductance and hence limited intrinsic gain of nMOS transistors. Because of this, the specification on the DC gain, that was initially set to 80 dB, has been downgraded to 70 dB.

#### Note

The specifications given in Table 3.1 are simplified specifications. They are mainly targeting the achievement of a certain gain-bandwidth product GBW and DC gain at lowest current consumption. The GBW sets the differential pair transconductance while the DC gain sets the output conductance. There is an additional specification on the random input-referred offset voltage which, if not met, might eventually require to increase the transistors area. There are no specifications on thermal noise since the transconductance is set by the GBW. There are no specifications on the flicker noise but if the corner frequency was set lower this would required to increase the transistors area. There are also no specifications on the slew-rate, which might be small because of the low-power objective. Finally, there are many more specifications such as CMRR, PSRR, input common-mode voltage range, output-voltage swing, etc... that are not discussed in this example.

Table 3.1: OTA specifications.

Specification	Symbol	Value	Unit
Minimum DC gain	$A_{dc}$	70	dB
Minimum gain-bandwidth product	GBW	1	MHz
Load capacitance	$C_L$	1	pF
Maximum input-referred random offset voltage	$V_{os}$	10	mV
Phase margin	PM	60	0

#### 3.2 Process

We will design the cascode gain stage for the open source IHP 13G2 BiCMOS process [2]. The physical parameters are given in Table 3.2, the global process parameters in Table 3.3 and finally the MOSFET parameters in Table 3.4.

## ⚠ Warning

The matching parameters for IHP  $130\mathrm{nm}$  are unknown. We will use those from a generic  $180\mathrm{nm}$  technology.

Table 3.2: Physical parameters

Parameter	Value	Unit
$\overline{T}$	300	K
$U_T$	25.865	mV

Table 3.3: Process parameters.

Parameter	Value	Unit	Comment
$t_{ox}$	2.24	nm	SiO <sub>2</sub> oxyde thickness
$C_{ox}$	15.413	$\frac{fF}{\mu m^2}$	Oxyde capacitance per unit area
$V_{DD}$	1.2	$\overline{V}$	Nominal supply voltage
$L_{min}$	130	nm	Minimum drawn gate length
$W_{min}$	150	nm	Minimum drawn gate width
$z_1$	340	nm	Minimum outer diffusion width
$z_2$	389	nm	Minimum diffusion width between two fingers

Table 3.4: Transistors parameters.

Paramet	ter nMOS	S pMOS	Unit
Length and width correction parameters for curre	ent		
I	DL = 59	51	nm
D	W -20	30	nm
ength and width correction for intrinsic and overlap capacitand	ces		
DLC		146	nm
DWC		15	nm
Length and width correction parameter for fringing capacitance			
DLGC		96	nm
DWGC		-15	nm
Long-channel sEKV parameters parameter			
	n 1.22	1.23	
$I_{spe}$		245	nA
	$T_{T0}$ 246	365	mV
Short-channel sEKV parameters parameter		24.0	
L	sat 7.1	24.9	nm V
T	$\lambda$ 1.375	6.078	$\frac{V}{\mu m}$
Junction capacitances parameter			fF
	$C_J = 0.976$		$\frac{J^{1}}{\mu m^{2}}$
$C_{JSWS}$	$T_{TI} = 0.025$	0.032	$\frac{fF}{\mu m}$
$C_{JSWG}$	AT = 0.03	0.027	$\frac{\frac{fF}{\mu m^2}}{\frac{fF}{\mu m}}$ $\frac{fF}{\mu m}$
Overlap capacitances paramete			
$C_G$	$a_{So} = 0.453$	0.443	$\frac{fF}{um}$
$C_G$		0.443	$\frac{\mu m}{fF} \ \frac{fF}{\mu m} \ \frac{fF}{\mu m}$
$C_G$		0.022	$rac{\mu m}{fF}$

Table 3.4: Transistors parameters.

Parameter	nMOS	pMOS	Unit
Fringing capacitances parameters			
$C_{GSf}$	0.2	0.1	$\frac{fF}{\mu m}$
$C_{GDf}$	0.2	0.1	$\frac{\mu m}{fF} \over \mu m}$
Flicker noise parameters			<i>p</i>
$K_F$	2.208e-24	1.2e-23	VAs
AF	1	1	-
ho	0.008642	0.04697	$\frac{Vm^2}{As}$
Matching parameters			
$A_{VT}$	5	5	$mV \cdot \mu m$
$A_eta$	1	1	$\% \cdot \mu m$

### 3.3 Design procedure

#### Important

For this process, the transistor dimensions are rounded to 10nm. We also will ignore the length and width reduction parameters DL and DW. The main reason is that most of the transistor length and width are sufficiently large that ignoring these parameters has little impact.

We start sizing the differential pair  $M_{1a}$ - $M_{1b}$ .

#### 3.3.1 Sizing the differential pair $M_{1a}$ - $M_{1b}$

In this example there is no specification on the thermal noise. Therefore the transconductance  $G_{m1}$  is set by the gain-bandwidth product according to

$$GBW = \frac{G_{m1}}{2\pi C_{out}},\tag{3.1}$$

where  $G_{m1}$  is the gate transconductance of  $M_{1a}$  and  $M_{1b}$  and  $C_{out}$  the total output capacitance

$$C_{out} = C_o + C_L \tag{3.2}$$

with  $C_o$  the parasitic capacitance at the output node and  $C_L$  the load capacitance.

In order to minimize the input-referred noise and offset, the input differential pair should be biased in weak inversion. The transconductance  $G_{m1}$  in deep weak inversion is then given by

$$G_{m1} = \frac{I_{b1}}{nU_T}. (3.3)$$

The bias current  $I_{b1}$  is the current flowing in each transistor  $M_{1a}$  and  $M_{1b}$  when the input differential voltage is zero. The bias current provided by  $M_{5b}$  is therefore  $2I_{b1}$ . The bias current must satisfy the following inequality:

$$I_{b1} \ge 2\pi n_{0n} U_T C_{out} GBW_{min}. \tag{3.4}$$

which for the given specifications gives  $I_{b1,min} = 198 \ nA$ . The corresponding slew-rate is then equal to  $SR_{min} = 198 \ mV/\mu s$  which we will consider as sufficient.

#### Important

If the slew-rate is not sufficient, the bias current  $I_b$  should be increased resulting in a higher current and power consumption. Other options include the use of a class AB OTA [5] or a dynamic/adaptive biasing OTA [6].

To have some margin to account for the additional parasitic capacitance at the output  $C_o$  due mostly to the junction capacitances that add to the load capacitance  $C_L$ , we set  $I_{b1} = 250~nA$  and the inversion coefficient to  $IC_1 = 0.1$ . The transconductance can be calculated from the  $G_m/I_D$  function as  $G_{m1} = 7.258~\mu A/V$ . This leads to a gain-bandwidth product GBW = 1.2~MHz, which is slightly higher than the target specification offering some margin. Knowing the drain current  $I_{D1}$  and the inversion coefficient, we can calculate the specific current  $I_{spec1} = 2.500~\mu A$  and the aspect ration  $W_1/L_1 = 3.5$ .

The degree of freedom left  $(W_1 \text{ or } L_1)$  can be determined by constraints either on the dc gain, the offset voltage or the flicker noise.

Before finalizing the sizing of the differential pair, we first will size the current mirror  $M_{3a}$ - $M_{3b}$  and the current sources  $M_{2a}$ - $M_{2b}$ - $M_{2c}$ .

## 3.4 Sizing of M<sub>3a</sub>-M<sub>3b</sub>

The current mirror  $M_{3a}$ - $M_{3b}$  should be biased as much in strong inversion as the voltage constraint allows for. We can set its  $V_{GS}$  voltage to the desired quiescent output voltage which we set to  $V_{GS3} = V_{outq} = V_{DD}/2 = 600 \ mV$ , which corresponds to an inversion coefficient  $IC_3 = 28.080$  and a saturation voltage  $V_{DSsat3} = 293 \ mV$ . We see that choosing a large IC and hence a large  $V_{GS}$  voltage comes at the cost of a large saturation voltage and hence a reduced output voltage swing. As discussed in the introduction we have chosen  $\alpha = 1.200$  so that  $I_{b3} = 300 \ nA$  and  $I_{b2} = I_{b1} + I_{b3} = 550 \ nA$ . Having set the inversion coefficient and bias current we can derive the specific current  $I_{spec3} = 10.68 \ nA$  and the aspect ration  $W_3/L_3 = 0.015$ . Having IC and  $I_D$ , we can deduce the transconductance  $G_{m3} = 1.633 \ \mu A/V$ .

We will now have to make sure that the non-dominant pole  $f_p$  at node 3 is sufficiently higher than the gain-bandwidth product GBW to insure the desired phase margin. The non-dominant pole is given

$$\omega_p = \frac{G_{m3}}{C_3},\tag{3.5}$$

where  $C_3$  is given by

$$C_3 = 2(C_{GS3} + C_{GB3}) (3.6)$$

Assuming that  $M_{3a}$ - $M_{3b}$  are in saturation, the gate-to-source capacitance  $C_{GS3}$  is given by

$$C_{GS3} \cong W_3 L_3 C_{ox} \cdot c_{qsi} + (C_{GSon} + C_{GSfn}) \cdot W_3, \tag{3.7}$$

where  $c_{gsi}$  is the intrinsic gate-to-source capacitance normalized to the total gate area  $W L C_{ox}$ , which is typically equal to 2/3 in strong inversion and is proportional to IC in weak inversion.

The gate-to-bulk capacitance  $C_{GB3}$  is given by

$$C_{GB3} \cong W_3 L_3 C_{ox} \cdot c_{abi} + C_{GBon} \cdot W_3, \tag{3.8}$$

where  $c_{gbi}$  is the gate-to-bulk intrinsic capacitance normalized to the total gate area  $W L C_{ox}$  and given by

$$c_{gbi} = \frac{n-1}{n} \cdot c_{gsi}. (3.9)$$

The capacitance at node 3 then scales with  $W_3$  and  $L_3$  according to

$$C_3 = W_3 L_3 \cdot C_{WL} + W_3 \cdot C_W, \tag{3.10}$$

with

$$C_{WL} = 2C_{ox} \cdot (c_{qsi} + c_{qbi}), \tag{3.11}$$

$$C_W = 2(C_{GSon} + C_{GSfn} + G_{GBon}). (3.12)$$

We already have set the inversion coefficient  $IC_3 = 28.080$ , from which we can calculate  $c_{gsi} = 0.600$  and  $c_{gbi} = 0.072$ . Since the W/L has already been set by the transconductance and the current, we can derive  $W_3$  and  $L_3$  for achieving a given capacitance  $C_3$  according to

$$W_3 = \frac{-C_W \cdot W_3 / L_3 + \sqrt{W_3 / L_3} \cdot \sqrt{4 C_3 C_{WL} + C_W^2 \cdot W_3 / L_3}}{2 C_{WL}},$$
(3.13)

$$L_3 = \frac{W_3}{W_3/L_3}. (3.14)$$

Setting the non-dominant pole  $f_p$  to 10 times the GBW, we get  $C_3 = 26$  fF,  $W_3 = 140$  nm and  $L_3 = 9.28 \ \mu m$ .

We see that  $W_3$  is smaller than the minimum width. If we don't want to increase  $W_3 L_3$  and hence  $C_3$ , we need to reduce the inversion coefficient  $IC_3$ . We can find the IC such that  $W_3 = W_{min}$  for the given  $f_p$  by looking at Figure 3.1.

 


Figure 3.1: Length  $L_3$  and width  $W_3$  of  $M_3$  versus  $IC_3$  for a given  $f_{p3}/GBW$  ratio.

We get  $IC_3 = 23.6$ ,  $W_3 = 150$  nm,  $L_3 = 8.35$   $\mu$ m,  $C_3 = 14.3$  fF,  $G_{m3} = 1.767$   $\mu$ A/V and  $I_{spec3} = 12.73$  nA. This leads to leading to the desired ratio  $f_p/GBW = 10.0$ .

The inversion coefficient of  $M_{3a}$ - $M_{3b}$  is therefore reduced from 28.1 to 23.6 in order to maintain a reasonable parasitic capacitance at node 3 to make sure that  $f_p$  is 10 times higher than the GBW.

Note that the  $V_{GS3}$  voltage has also dropped to  $V_{GS3} = 569 \ mV$ , so that the quiescent output voltage is now lower than  $V_{outq} = V_{DD}/2 = 600 \ mV$ . We might need to introduce an offset voltage to shift the output back to  $V_{outq}$  (in the high gain region). On the other hand the saturation voltage is now also lower  $V_{DSsat3} = 272 \ mV$  improving the output swing.

## 3.5 Sizing of $M_{4a}$ - $M_{4b}$ and $M_{5a}$ - $M_{5b}$

The cascode transistors are sized according to the desired DC gain given by

$$A_{dc} = \frac{G_{m1}}{G_o} \tag{3.15}$$

where  $G_o$  is the conductance at the output node given by

$$G_o \cong G_{o35} + G_{o124} \tag{3.16}$$

where

$$G_{o35} \triangleq \frac{G_{ds3} G_{ds5}}{G_{ms5}},\tag{3.17}$$

$$G_{o35} \triangleq \frac{G_{ds3} G_{ds5}}{G_{ms5}},$$

$$G_{o124} \triangleq \frac{(G_{ds1} + G_{ds2}) G_{ds4}}{G_{ms4}}.$$
(3.17)

The minimum DC gain specification is given by  $A_{dc} = 3.2 \text{e} + 03$  or  $A_{dc} = 70$  dB. We can then deduce the output conductance  $G_o = 2295.104 \frac{pA}{V}$ . We will split the output conductance  $G_o$  equally between the nMOS and pMOS cascodes.

To minimize the saturation voltage and maximize the current efficiency, the cascode transistors  $M_{4a}$ - $M_{4b}$ and  $M_{5a}$ - $M_{5b}$  are biased in weak inversion. We choose their inversion coefficient as  $IC_5 = IC_4 = 0.1$ , which gives a saturation voltage  $V_{DSsat5} = V_{DSsat4} = 105 \text{ mV}$ . Having set the inversion coefficient and knowing the bias current, we can deduce the specific current  $I_{spec4} = 3.0 \ \mu A$  and the aspect ratio  $W_4/L_4 = 12.265$  for  $M_{4a}$ - $M_{4b}$  and  $I_{spec5} = 3.0 \ \mu A$  and  $W_5/L_5 = 4.235$  for  $M_{5a}$ - $M_{5b}$ .

We can now calculate the source transconductances that are needed for the calculation of the output conductances  $G_{ms4} = 10.625 \ \mu A/V$  and  $G_{ms5} = 10.625 \ \mu A/V$ . Having already the length of  $M_{3a}$ - $M_{3b}$ , we can estimate its output conductance  $G_{ds3} = 26.130 \ nA/V$ . We can then deduce the output conductance of  $M_{5a}$ - $M_{5b}$   $G_{ds5} = 466.6$  nA/V, which corresponds to a cascode gain  $G_{ms5}/G_{ds5} = 22.8$ . We can then deduce the length of  $M_{5a}$ - $M_{5b}$  from  $G_{ds5}$  as  $L_5 = 468 \ nm$ .

Because of the high output conductance of nMOS transistor we increase the length of  $M_{5a}$ - $M_{5b}$  to  $L_5 = 2.00 \ \mu m$ . Keeping the same W/L we get the width  $W_5 = 8.47 \ \mu m$ .

We can recalculate the contribution of  $M_{3a}$ - $M_{3b}$  and  $M_{5a}$ - $M_{5b}$  to the total output conductance  $G_{o35}$  = 268.3 pA/V and deduce the remaining contribution allocated to  $M_{1a}$ - $M_{1b}$ ,  $M_{2b}$ - $M_{2c}$  and  $M_{4a}$ - $M_{4b}$  $G_{o124} = 2.0 \ nA/V.$ 

At this point we don't know the lengths neither of  $M_{1a}$ - $M_{1b}$  nor of  $M_{2b}$ - $M_{2c}$  and  $M_{4a}$ - $M_{4b}$ . We can choose that  $G_{ds1} + G_{ds2} = G_{ds4}$  and  $G_{ds1} = G_{ds2}$  so that  $G_{ds1} = G_{ds2} = G_{ds4}/2$ . We can then deduce the output conductance of  $M_{4a}$ - $M_{4b}$   $G_{ds4} = 146.751 \frac{nA}{V}$  from which we get the length  $L_4 = 340 \text{ nm}$ and width  $W_4 = 4.17 \ \mu m$ .

This might not be long enough. To secure enough margin for the DC gain we set  $L_4 = 1.30 \ \mu m$ which, for the same W/L, gives a width  $W=15.94 \ \mu m$ . The cascode voltage gain is then given by  $G_{ms4}/G_{ds4} = 279.9$ . We can deduce the length of  $M_{1a}$ - $M_{1b}$  and  $M_{2b}$ - $M_{2c}$  accounting for the different currents flowing in  $M_{4a}$ - $M_{4b}$ ,  $M_{1a}$ - $M_{1b}$  and  $M_{2b}$ - $M_{2c}$   $L_1 = 9.58 \ \mu m$  and  $L_2 = 4.77 \ \mu m$ .

We can now finalize the sizing of  $M_{1a}$ - $M_{1b}$  with  $W_1 = 33.81 \ \mu m$ .

This is a very wide transistor. We will reduce it by reducing the length to  $L_1 = 3.00 \ \mu m$ . Keeping the same W/L we get the width  $W_1 = 10.59 \ \mu m$ . We can re-calculate the theoretical DC gain  $A_{dc} =$ 1.3e+04 (estimation) or  $A_{dc} = 82 \text{ dB}$  (estimation).

## 3.6 Sizing of $M_{2a}$ - $M_{2b}$ - $M_{2c}$

To size  $M_{2b}$ - $M_{2c}$  we will choose its saturation voltage to  $V_{SDsat2} = 200~mV$  in order to maximize the output swing. This leads to an inversion coefficient  $IC_2 = 10.948$ , a specific current  $I_{spec2} = 0.050~\mu A$  and an aspect ratio  $W_2/L_2 = 0.205$ . Knowing  $L_2 = 4.77~\mu m$  we deduce  $W_2 = 980~nm$ .

The contribution to the input-referred noise PSD of  $M_{2b}$ - $M_{2c}$  can be quite large compared to that of the differential pair  $M_{1a}$ - $M_{1b}$  because the current  $I_{b2}$  is at least two times  $I_{b1}$ . It is therefore hard to make  $G_{m2}$  much smaller than  $G_{m1}$  without drastically increasing IC and hence  $V_{DSsat}$  and loosing output swing. We can check the contribution of  $M_{2a}$ - $M_{2b}$ - $M_{2c}$  to the input-referred noise. If  $M_{2a}$ - $M_{2b}$ - $M_{2c}$  are perfectly matched, the noise produced by  $M_{2a}$  is canceled out at the output and can therefore be neglected. Since the noise is usually dominated by the flicker noise we can calculate the contribution of  $M_{2b}$ - $M_{2c}$  to the input-referred flicker noise relative to the contribution of the differential pair  $M_{1a}$ - $M_{1b}$ 

$$\eta_{fl}|_{M_{2b}-M_{2c}} = \frac{\rho_p}{\rho_n} \left(\frac{G_{m2}}{G_{m1}}\right)^2 \frac{W_1 L_1}{W_2 L_2}$$
(3.19)

We get  $\eta_{fl}|_{M_{2b}-M_{2c}} = 13.842$  which is very large.

We can increase the length and width by a factor 2 resulting in  $W_2 = 1.96 \ \mu m$  and  $L_2 = 9.54 \ \mu m$  which reduces  $\eta_{fl}|_{M_{2b}-M_{2c}}$  to 3.531.

We can also check the contribution of  $\mathrm{M}_{3a}\text{-}\mathrm{M}_{3b}$  to the input-referred noise by calculating

$$\eta_{fl}|_{M_{3a}-M_{3b}} = \left(\frac{G_{m3}}{G_{m1}}\right)^2 \frac{W_1 L_1}{W_3 L_3}$$
(3.20)

which is equal to 11.344.

## 3.7 Sizing $M_{7a}$ - $M_{7b}$

The size of  $M_{7a}$ - $M_{7b}$  is conditioned by the minimum input common-mode voltage  $V_{ic,min}$ 

$$V_{ic,min} = V_{GS1} + V_{DSsat7}. (3.21)$$

The gate-to-source voltage  $V_{GS1}$  is given by

$$V_{GS1} = V_{T0n} + (n_{0n} - 1) V_{S1} + n_{0n} U_T (v_p - v_s)$$
(3.22)

Unfortunately, at this point we don't know the value of the source voltage  $V_{S1}$  of  $M_{1a}$ - $M_{1b}$  (voltage at common-source node 1). In weak inversion  $v_p - v_s \cong 0$  so that

$$V_{GS1} \cong V_{T0n} + (n_{0n} - 1) V_{S1} \tag{3.23}$$

Since we don't know  $V_{S1}$  we can approximate  $V_{GS1}$  by  $V_{T0n}=246~mV$ . If we set the minimum input common-mode voltage to  $V_{ic,min}=0.5~V$ , it results in a saturation voltage voltage for  $M_{7a}$ - $M_{7b}$  equal to  $V_{DSsat7}=254~mV$ , which corresponds to an inversion coefficient  $IC_7=20.1$ . Having the IC and the current we can derive the specific current  $I_{spec7}=25~nA$  and the aspect ratio  $W_7/L_7=0.035$ . Since the W/L is small, we need to set the width to  $W_7=W_{min}=150~nm$  resulting in a length  $L_7=4.27~\mu m$ .

We now need to set the bias voltages  $V_{b1}$  and  $V_{b2}$ .

## **3.8** Bias voltages $V_{b1}$ and $V_{b2}$

We still need to calculate the required bias voltages  $V_{b1}$  for  $M_{5a}$ - $M_{5b}$  and  $V_{b2}$  for  $M_{4a}$ - $M_{4b}$ .

We start calculating the maximum bias voltage  $V_{b2,max}$  still keeping  $M_{2a}$ - $M_{2b}$  in saturation

$$V_{b2,max} = V_{DD} - V_{SG4} - V_{SDsat2} (3.24)$$

The saturation voltage of  $M_{2a}$ - $M_{2b}$  is given by  $IC_2$  as  $V_{SDsat2} = 200 \ mV$ . The source-to-gate voltage  $V_{SG4}$  is given by

$$V_{SG4} = V_{T0p} + (n_{0p} - 1) V_{BS4} + n_{0p} U_T (v_p - v_s)$$
(3.25)

In weak inversion  $v_p - v_s \cong 0$  and therefore

$$V_{SG4} \cong V_{T0p} + (n_{0p} - 1) V_{BS4} \tag{3.26}$$

However, at this point we don't know the source voltage of  $M_{4a}$ - $M_{4b}$ . We can estimate that  $V_{SG4} \cong V_{T0p} = 365 \ mV$  which results in  $V_{b2,max} = 635 \ mV$ .

We also want to make sure that the  $V_{SD}$  voltage across  $M_{4a}$ - $M_{4b}$  is large enough not to degrade the output conductance. We can choose  $V_{SD4} = 200 \ mV$ , which gives  $V_{b2,min} = 404 \ mV$ .

The maximum value of  $V_{b1}$  is set by keeping a sufficient  $V_{DS}$  voltage for  $M_{5a}$ - $M_{5b}$ 

$$V_{b1,max} = V_{GS5} - V_{DS5} + V_{GS3} (3.27)$$

where

$$V_{GS5} = V_{T0n} + (n_{0n} - 1) V_{SB5} + n_{0n} U_T (v_p - v_s) \cong V_{T0n} + (n_{0n} - 1) V_{SB5} \cong V_{T0n}.$$
(3.28)

If we choose  $V_{DS5} = 200 \ mV$ , we get  $V_{b1,max} = 615 \ mV$ .

The minimum  $V_{b1}$  voltage is set by keeping  $M_{3a}$ - $M_{3b}$  in saturation

$$V_{b1.min} = V_{GS5} + V_{DSsat3} (3.29)$$

resulting in  $V_{b1,min} = 518 \ mV$ .

So the bias voltages  $V_{b1}$  and  $V_{b2}$  shuld satisfy the following inequalities

$$0.518 \ V \le V_{b1} \le 0.615 \ V$$
 and

$$0.404 \ V \le V_{b2} \le 0.635 \ V$$

We finally choose  $V_{b1} = 0.550 V$  and  $V_{b2} = 0.450 V$ .

The sizing process is now completed. The transistor sizes and bias are summarized below.

## 3.9 Summary

#### 3.9.1 Specifications

The specifications are recalled in Table 3.5.

Table 3.5: OTA specifications.

Specification	Symbol	Value	Unit
Minimum DC gain	$A_{dc}$	70	dB
Minimum gain-bandwidth product	GBW	1	MHz

Table 3.5: OTA specifications.

Specification	Symbol	Value	Unit
Load capacitance	$C_L$	1	pF
Maximum input-referred random offset voltage	$V_{os,max}$	10	mV
Phase margin	PM	60	0

#### 3.9.2 Bias

The bias information are summarized in Table 3.6.

Table 3.6: OTA bias.

Bias voltage or current	Symbol	Value	Unit
Supply voltage	$V_{DD}$	1.20	$\overline{V}$
Bias current	$I_{b1}$	250.00	nA
Bias current	$I_{b2}$	550.00	nA
Cascode bias voltage	$V_{b1}$	0.55	V
Cascode bias voltage	$V_{b2}$	0.45	V

#### 3.9.3 Transistor information

The transistor sizes and large-signal variables are summarized in Table 3.7, whereas Table 3.8 gives the small-signal and thermal noise parameters. An Excel table is generated with more information (e.g. all the parasitic capacitances).

Table 3.7: Transistor size and bias information.

Transistor	$W$ [ $\mu m$ ]	$L [\mu m]$	$I_D [nA]$	$I_{spec} [nA]$	IC	$V_G - V_{T0} [mV]$	$V_{DSsat} [mV]$
M1a	10.59	3.00	250	2500	0.1	-47	105
M1b	10.59	3.00	250	2500	0.1	-47	105
M2a	3.92	9.54	1100	101	10.9	142	200
M2b	1.96	9.54	550	50	10.9	142	200
M2c	1.96	9.54	550	50	10.9	142	200
M3a	0.15	8.35	300	13	23.6	217	272
M3b	0.15	8.35	300	13	23.6	217	272
M4a	15.94	1.30	300	2999	0.1	-46	105
M4b	15.94	1.30	300	2999	0.1	-46	105
M5a	8.47	2.00	300	3000	0.1	-47	105
M5b	8.47	2.00	300	3000	0.1	-47	105
M7a	0.15	4.27	500	25	20.1	199	254
M7b	0.15	4.27	500	25	20.1	199	254

Table 3.8: Transistor small-signal and thermal noise parameters.

Transistor	$G_{spec} \left[ \mu A/V \right]$	$G_{ms} \left[ \mu A/V \right]$	$G_m \left[ \mu A/V \right]$	$G_{ds} [nA/V]$	$\gamma_n$
M1a	96.668	8.855	7.258	60.606	0.627
M1b	96.668	8.855	7.258	60.606	0.627
M2a	3.886	11.058	8.991	18.971	0.767

Table 3.8: Transistor small-signal and thermal noise parameters.

Transistor	$G_{spec} \left[ \mu A/V \right]$	$G_{ms} \left[ \mu A/V \right]$	$G_m \left[ \mu A/V \right]$	$G_{ds} [nA/V]$	$\gamma_n$
M2b	1.943	5.529	4.495	9.485	0.767
M2c	1.943	5.529	4.495	9.485	0.767
M3a	0.492	2.155	1.767	26.130	0.776
M3b	0.492	2.155	1.767	26.130	0.776
M4a	115.955	10.625	8.638	37.968	0.632
M4b	115.955	10.625	8.638	37.968	0.632
M5a	115.974	10.625	8.709	109.091	0.627
M5b	115.974	10.625	8.709	109.091	0.627
M7a	0.962	3.858	3.162	85.161	0.773
M7b	0.962	3.858	3.162	85.161	0.773

## **4 OTA Characteristics**

In this section, we check whether the specs are achieved.

### 4.1 Open-loop gain

We can calculate the various OTA features related to the open-loop transfer function, which are given in Table 4.1.

Symbol	Theoretical Value	Unit
$\overline{A_{dc}}$	82.917	dB
$G_{m1}$	7.258	$\mu A/V$
$G_{m2}$	4.495	$\mu A/V$
$G_{m3}$	1.767	$\mu A/V$
$G_{ms4}$	10.625	$\mu A/V$
$G_{ms5}$	10.625	$\mu A/V$
$G_{ds1}$	60.606	nA/V
$G_{ds2}$	9.485	nA/V
$G_{ds3}$	26.130	nA/V
$G_{ds4}$	37.968	nA/V
$G_{ds5}$	109.091	nA/V
$C_3$	25.931	fF
$C_4$	96.248	fF
$f_0$	80.694	Hz
$\overrightarrow{GBW}$	1.129	MHz
$f_p$	10.843	MHz
$f_z$	21.686	MHz
$f_{p4}$	17.570	MHz

Table 4.1: OTA gain variables.

The gain-bandwidth product from the specifications is repeated here

GBW = 1.000 MHz (from spec).

The estimate value assuming that all the non-dominant poles are much higher than the GBW is given by

 $GBW_{est} = 1.129 \text{ MHz (estimation)}.$ 

The GBW accounting for the effect of the additional non-dominant poles is given by

 $GBW_{the} = 1.122 \text{ MHz (theory)}.$ 

We see that there is only a small difference between  $GBW_{est}$  and  $GBW_{the}$ , which confirms that the non-dominant poles are sufficiently far from GBW as stated in Table 4.1.

We can now plot the gain response Using the variables given in Table 4.1. It is shown in Figure 4.1.

From Figure 4.1, we see that the GBW and DC gain are met.

 


Figure 4.1: OTA theoretical transfer function.

We can now have a look at the input-refrred noise PSD.

## 4.2 Input-referred noise

We can now compute all the parameters needed for the calculation of the OTA thermal noise excess factor and its input-referred thermal noise PSD and resistance. They are given in Table 4.2.

Table 4.2: OTA thermal noise parameters.

Symbol	Theoretical Value	Unit
$G_{m1}$	7.258	$\mu A/V$
$G_{m2}$	4.495	$\mu A/V$
$G_{m3}$	1.767	$\mu A/V$
$G_{m1}/G_{m2}$	1.615	-
$G_{m1}/G_{m3}$	4.108	-
$\gamma_{n1}$	0.627	-
$\gamma_{n2}$	0.767	-
$\gamma_{n3}$	0.776	-
$\eta_{th}$	1.058	-
$\gamma_{ota}$	2.581	-
$R_{nt}$	355.675	$k\Omega$
$S_{ninth}$	5.9e-15	$V^2/Hz$
$\sqrt{S_{ninth}}$	76.783	$nV/\sqrt{Hz}$
$10 \cdot \log(S_{ninth})$	-142.295	$dBv/\sqrt{Hz}$

From Table 4.2, we see that the contribution of  $M_{2b}$ - $M_{2c}$  and  $M_{3a}$ - $M_{3b}$  is only 1.058 that of  $M_{1a}$ - $M_{1b}$ . This leads to an OTA thermal noise excess factor  $\gamma_{n,ota} = 2.581$ , which is 2.1 times larger than that of the differential pair  $2\gamma_{n1} = 1.254$ .

We can now compute all the parameters needed for the calculation of the input-referred flicker noise and the corner frequency. They are given in Table 4.3.

Symbol	Theoretical Value	Unit
$\overline{(G_{m1}/G_{m2})^2}$	2.6	-
$(G_{m1}/G_{m3})^2$	16.9	-
$ ho_p/ ho_n$	5.4	-
$\frac{W_1 \cdot L_1}{W_2 \cdot L_2}$	1.7	-
$egin{array}{c} \overline{W_2 \cdot L_2} \\ \underline{W_1 \cdot L_1} \\ \overline{W_3 \cdot L_3} \end{array}$	29.6	-
$\eta_{fl}$	5.284	-
$\sqrt{S_{min} g_I(1 Hz)}$	7.5	$\mu V/\sqrt{Hz}$

Table 4.3: OTA flicker noise parameters.

As desired, from Table 4.3, we see that the contribution of  $M_{2b}$ - $M_{2c}$  and  $M_{3a}$ - $M_{3b}$  to the flicker noise is only 5.284 that of  $M_{1a}$ - $M_{1b}$ . It is sligthly lower than the value obtained in the design phse simply because the calculations use the effective width and length.

-102.5 9

We can plot the input-reffered noise which is shown in Figure 4.2.

 $10 \cdot \log(S_{ninfl}(1 Hz))$ 

 $f_k$ 

 


Figure 4.2: OTA theoretical input-referred noise PSD.

## 4.3 Input-referred offset

The variance of the input-referred offset voltage is given by (2.32), which is repeated below

$$\sigma_{V_{os}}^2 = \sigma_{V_T}^2 + \sigma_{\beta}^2. \tag{4.1}$$

 $dBv/\sqrt{Hz}$ 

kHz

 $\sigma_{V_T}^2$  is the  $V_T$ -mismatch given by

$$\sigma_{V_T}^2 = \sigma_{V_{T1}}^2 \cdot (1 + \xi_{V_T}) \tag{4.2}$$

where

$$\xi_{V_T} = \left(\frac{G_{m2}}{G_{m1}}\right)^2 \left(\frac{A_{V_{T_p}}}{A_{V_{T_p}}}\right)^2 \frac{W_1 L_1}{W_2 L_2} + \left(\frac{G_{m3}}{G_{m1}}\right)^2 \frac{W_1 L_1}{W_3 L_3} \tag{4.3}$$

represents the  $V_T$ -mismatch contributions to the input-referred offset of the current source  $M_{2b}$ - $M_{2c}$  and current mirror  $M_{3a}$ - $M_{3b}$  relative to that of the differential pair.

 $\sigma_{\beta}^2$  is the  $\beta$ -mismatch given by

$$\sigma_{\beta}^2 = \left(\frac{I_{b1}}{G_{m1}}\right)^2 \cdot \sigma_{\beta_1}^2 \cdot (1 + \xi_{\beta}) \tag{4.4}$$

where

$$\xi_{\beta} = \left(\frac{I_{b2}}{I_{b1}}\right)^2 \left(\frac{A_{\beta_p}}{A_{\beta_n}}\right)^2 \frac{W_1 L_1}{W_2 L_2} + \left(\frac{I_{b3}}{I_{b1}}\right)^2 \frac{W_1 L_1}{W_2 L_2}.$$
 (4.5)

The parameter for calculating the standard deviation of the input-referred offset voltage are given in Table 4.4.

Table 4.4: OTA input-referred offset parameters.

Symbol	Theoretical Value	Unit
$\sigma_{VT1}$	0.887	$\overline{mV}$
$\sigma_{VT2}$	1.156	mV
$\sigma_{VT3}$	4.468	mV
$\sigma_{eta 1}$	0.177	%
$\sigma_{eta 2}$	0.231	%
$\sigma_{eta 3}$	0.894	%
$(G_{m2}/G_{m1})^2$	0.384	-
$(G_{m3}/G_{m1})^2$	0.059	-
$W_1 L_1/(W_2 L_2)$	1.699	-
$W_1 L_1/(W_3 L_3)$	25.365	-
$(I_{b2}/I_{b1})^2$	4.840	-
$(I_{b3}/I_{b1})^2$	1.440	-
$\xi_{VT}$	2.155	-
$\xi_eta$	44.750	-
$\sigma_{V_T}^2$	2.482	$mV^2$
$\sigma_{V_T}$	1.576	mV
$\sigma_{eta}^{ar{2}}$	0.171	$mV^2$
$\sigma_{eta}$	0.413	mV
$\sigma_{Vos}$	1.629	mV

From Table 4.4 and contrary to the other OTA, we see that in the case of the folded cascode OTA the  $\beta$ -mismatch cannot be neglected. This is mostly because of the  $W_1 L_1/(W_3 L_3)$  ratio equal to 25.365.

## 4.4 Current and power consumption

The total current consumption, ignoring the current drawn by  $M_{2a}$  and  $M_{7a}$ , is  $I_{tot} = 2I_{b2} = 1.1 \ \mu A$  and the power consumption is  $P = 1.320 \ \mu W$ .

Assuming the input differential pair  $M_{1a}$ - $M_{1b}$  is biased in deep weak inversion, the minimum bias current  $I_{b1,min}$  is directly related to the gain-bandwidth product GBW according to

$$I_{b1,min} \cong nU_T \cdot C_L \cdot \omega_u = nU_T \cdot C_L \cdot 2\pi \, GBW, \tag{4.6}$$

which is equal to 198 nA. The minimum total current consumption assuming  $\alpha \triangleq I_{b3}/I_{b1} = 1.2$  can then be estimated as  $I_{tot,min} \cong 2I_{b2,min} = 2(I_{b1,min} + I_{b3,min}) = 2I_{b1,min} (1 + \alpha) = 872 \ nA$ . The actual current consumption accounting for some margin taken on the GBW is therefore 26% higher than the minimum.

The current consumption of the folded cascode OTA is 2.2 times larger than that of the telescopic OTA for the same specifications.

#### Note

Note that the telescopic OTA is the differential OTA that has the minimum power consumption for similar gain-bandwidth product, DC gain and phase margin specifications. Of course it has the smallest input and output voltage swings.

The above design will now be checked against simulations.

## 5 Simulation results from ngspice

The theoretical results can be validated with the results obtained from simulations performed with ngspice. In order to run the simulations you need to have ngspice correctly installed. Please refer to the installation instructions.

#### Note

The simulations are performed with the PSP 103.6 compact model [4] using the parameters from the IHP open source PDK [2]. For ngspice, we use the Verilog-A implementation given in the IHP package [2] and compiled the OSDI file with OpenVAF [7] to run with ngspice [8]. In addition to the PSP user manual [4] a documentation of PSP and other MOSFET compact models and their parameter extraction can be found in [9].

## 5.1 Operating point

We first write the parameter file for this specific design for running the ngspice simulations. Before running the AC and NOISE simulations, we first need to check the quiescent voltages and currents and the operating points of all transistors by running a .OP simulation.

Table 5.1: OTA node voltages with the OTA in open-loop without offset correction.

Node	Voltage
vdd	1.2
vb1	0.55
vb2	0.45
inp	0.6
$_{ m inn}$	0.6
out	0.528168
ic	0.6
$\operatorname{id}$	0
1	0.421646
2	0.607732
3	0.51668
4	0.823598
5	0.82362
6	0.352809
7	0.353196
8	0.487271

We can extract the OTA quiescent node voltages from the ngspice .ic file. They are presented in Table 5.1. We see that the simulated quiescent output voltage is  $V_{outq} = 528 \ mV$ . This is fine and the OTA is biased in the high gain region. Similarly to the telescopic OTA, the quiescent output voltage is actually set by the  $V_{GS}$  voltage of  $M_{3a}$ . Indeed, if perfect matching is assumed (which is the case in the simulation), since  $M_{5a}$ - $M_{5b}$  have the same drain current and share the same gate voltage, they

have the same  $V_{GS}$  voltage and also have the same drain voltage. We therefore don't need to extract any offset voltage at this point and can proceed with the simulation of the large-signal characteristic.

The operating point information for all transistors are extracted from the ngspice .op file. The data is split into the large-signal operating informations in Table 5.2, the small-signal operating point informations in Table 5.3 and the noise operating point informations in Table 5.4.

Table 5.2: Operating point information extracted from ngspice .op file for each transistor.

Transistor	$I_D [nA]$	$V_{GS}$ $[mV]$	$V_{DS}$ $[mV]$	$V_{SB}$ $[mV]$	$V_{GS} - V_T [mV]$	$V_{Dsat} [mV]$
M1a	247.977	178	402	422	-51	109
M1b	247.981	178	402	422	-51	109
M2a	1099.885	592	592	-0	250	232
M2b	574.355	592	376	-0	251	233
M2c	574.354	592	376	-0	251	233
M3a	326.339	517	353	0	355	300
M3b	326.357	517	353	0	355	300
M4a	326.358	374	307	376	-37	106
M4b	326.353	374	295	376	-37	106
M5a	326.334	197	164	353	-42	110
M5b	326.352	197	175	353	-43	110
M7a	499.992	487	487	0	313	272
M7b	495.960	487	422	0	313	272

Table 5.3: PSP small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$G_m \left[ \mu A/V \right]$	$G_{mb} \left[ \mu A/V \right]$	$G_{ds} [nA/V]$
M1a	7.529	0.773	202.371
M1b	7.529	0.773	202.369
M2a	8.218	1.626	17.100
M2b	4.273	0.840	21.518
M2c	4.273	0.840	21.522
M3a	1.880	0.261	47.519
M3b	1.881	0.261	47.338
M4a	9.512	1.524	21.115
M4b	9.508	1.523	21.999
M5a	9.711	1.067	378.445
M5b	9.715	1.065	376.234
M7a	3.256	0.447	58.346
M7b	3.232	0.444	64.920

Table 5.4: PSP noise operating point information extracted from ngspice .op file for each transistor.

Transistor	$S_{ID,th} [A^2/Hz]$	$S_{ID,fl}$ at 1Hz $[A^2/Hz]$
M1a	7.501e-26	2.857e-22
M1b	7.501e-26	2.857e-22
M2a	1.995e-25	1.481e-21
M2b	1.039e-25	8.116e-22
M2c	1.039e-25	8.116e-22
M3a	2.397e-26	7.247e-22

Table 5.4: PSP noise operating point information extracted from ngspice .op file for each transistor.

Transistor	$S_{ID,th} [A^2/Hz]$	$S_{ID,fl}$ at 1Hz $[A^2/Hz]$
M3b	2.397e-26	7.249e-22
M4a	1.837e-25	2.308e-21
M4b	1.837e-25	2.309e-21
M5a	9.724 e-26	1.080e-21
M5b	9.728e-26	1.068e-21
M7a	4.098e-26	4.086e-21
M7b	4.066e-26	4.039e-21

Table 5.5: sEKV parameters calculated from the values extracted from the simulation to compare with Table 3.7.

Transistor	$W_{eff} [\mu m]$	$L_{eff} [\mu m]$	$W_{eff}/L_{eff}$	$I_{spec} [\mu A]$	$\overline{IC}$
M1a	10.610	2.941	3.607	2.555	0.097
M1b	10.610	2.941	3.607	2.555	0.097
M2a	3.890	9.586	0.406	0.099	11.081
M2b	1.930	9.586	0.201	0.049	11.663
M2c	1.930	9.586	0.201	0.049	11.663
M3a	0.170	8.291	0.021	0.015	22.471
M3b	0.170	8.291	0.021	0.015	22.472
M4a	15.910	1.344	11.839	2.896	0.113
M4b	15.910	1.344	11.839	2.896	0.113
M5a	8.490	1.941	4.374	3.098	0.105
M5b	8.490	1.941	4.374	3.098	0.105
M7a	0.170	4.211	0.040	0.029	17.486
M7b	0.170	4.211	0.040	0.029	17.345

Table 5.6: sEKV small-signal parameters calculated from the values extracted from the simulation to compare with Table 3.8.

Transistor	$G_{spec} \left[ \mu A/V \right]$	n	$G_m \left[ \mu A/V \right]$	$G_{ms} \left[ \mu A/V \right]$	$G_{ds} [nA/V]$
M1a	98.788	1.103	7.529	8.302	202.371
M1b	98.788	1.103	7.529	8.302	202.369
M2a	3.838	1.198	8.218	9.844	17.100
M2b	1.904	1.197	4.273	5.113	21.518
M2c	1.904	1.197	4.273	5.113	21.522
M3a	0.561	1.139	1.880	2.142	47.519
M3b	0.561	1.139	1.881	2.142	47.338
M4a	111.958	1.160	9.512	11.036	21.115
M4b	111.958	1.160	9.508	11.031	21.999
M5a	119.772	1.110	9.711	10.778	378.445
M5b	119.772	1.110	9.715	10.780	376.234
M7a	1.105	1.137	3.256	3.703	58.346
M7b	1.105	1.137	3.232	3.676	64.920

Table 5.7: sEKV noise parameters calculated from the values extracted from the simulation to compare with Table 4.2.

Transistor	$\sqrt{S_{nin,th}} \left[ nV/\sqrt{Hz} \right]$	$R_{nin,th} [k\Omega]$	$\gamma_n [-]$	$\sqrt{S_{nin,fl}} [nV/\sqrt{Hz}]$
M1a	36.378	79.834	0.601	2244.920
M1b	36.377	79.833	0.601	2244.902
M2a	54.354	178.229	1.465	4683.598
M2b	75.427	343.223	1.466	6667.880
M2c	75.427	343.224	1.466	6667.882
M3a	82.342	409.033	0.769	14316.833
M3b	82.333	408.942	0.769	14316.983
M4a	45.055	122.461	1.165	5050.903
M4b	45.073	122.561	1.165	5054.063
M5a	32.111	62.206	0.604	3383.623
M5b	32.106	62.186	0.604	3363.983
M7a	62.167	233.152	0.759	19630.733
M7b	62.384	234.783	0.759	19663.094

Table 5.8: Bias voltages and operating regions extracted from ngspice for each transistor.

Trans.	Type	Funct.	$V_G[V]$	$V_S[V]$	$V_D[V]$	$V_{DS}$ $[mV]$	$V_{DSsat} [mV]$	Reg.	Sat.
M1a	n	DP	0.600	0.422	0.824	402	109	WI	sat
M1b	n	DP	0.600	0.422	0.824	402	109	WI	$\operatorname{sat}$
M2a	p	CM	0.592	0.000	0.592	592	232	$\operatorname{SI}$	$\operatorname{sat}$
M2b	p	CM	0.592	0.000	0.376	376	233	$\operatorname{SI}$	$\operatorname{sat}$
M2c	p	CM	0.592	0.000	0.376	376	233	$\operatorname{SI}$	$\operatorname{sat}$
M3a	n	CM	0.517	0.000	0.353	353	300	$\operatorname{SI}$	$\operatorname{sat}$
M3b	$\mathbf{n}$	CM	0.517	0.000	0.353	353	300	$\operatorname{SI}$	sat
M4a	p	CA	0.750	0.376	0.683	307	106	MI	sat
M4b	p	CA	0.750	0.376	0.672	295	106	MI	$\operatorname{sat}$
M5a	$\mathbf{n}$	CA	0.550	0.353	0.517	164	110	MI	sat
M5b	n	CA	0.550	0.353	0.528	175	110	MI	sat
M7a	n	CM	0.487	0.000	0.487	487	272	$\operatorname{SI}$	$\operatorname{sat}$
M7b	n	CM	0.487	0.000	0.422	422	272	SI	sat

From Table 5.1, we see that all transistors have a sufficiently large  $V_{DS}$  voltage and are therefore biased in saturation. Additionally we see that all the saturation voltages are summing up to 749 mV leaving an output voltage swing equal to  $V_{out,swing} = 451 \ mV$ .

From Table 5.3, we see that the output conductance of  $M_{5a}$ - $M_{5b}$  is very large (much larger than the theoretical estimation) despite we have chosen a very long transistor  $L_5 = 2.00 \ \mu m$ . This will impact the small-signal DC gain as shown below.

The data extracted from the operating point simulation can be translated into sEKV parameters. Table 5.5 presents the effective width and length, the specific current and the resulting inversion coefficient which can be compared to the values resulting from the design given in Table 3.7. We observe that the values are close.

Table 5.6 presents the sEKV parameters including the specific conductance  $G_{spec}$ , slope factor n, gate transconductance  $G_m$ , source transconductance  $G_{ms}$  and output conductance  $G_{ds}$ . They can be compared to the results of the design presented in Table 3.8. Again, we see that the simulated values of the transconductances are close to the theoretical estimation. However, the simulated values of the

output conductances are much larger than the estimated values, explaining why the estimated DC gain is much larger than the simulated value.

Table 5.7 presents the sEKV noise parameters. We can observe that the thermal noise excess factors of pMOS transistors are larger than the estimated values shown in Table 4.2.

Finally we can check whether all transistors are biased in saturation. From Table 5.8, we see that all transistors are biased in saturation. The operating points look fine. We can now proceed with the simulation of the open-loop large-signal transfer characteristic.

### 5.2 Large-signal differential transfer characteristic

We now simulate the DC differential transfer characteristic. The simulation of the large-signal inputoutput characteristic is presented in Figure 5.1.

 


Figure 5.1: Simulated large-signal input-output characteristic.

From Figure 5.1, we see that the output swing is about  $V_{out,swing} = 450 \ mV$ , which corresponds to the above estimation. We can now zoom into the high gain region in order to extract the offset voltage that is needed to bring the output voltage back to  $V_{outq} = 0.600 \ V$ . The simulation results are presented in Figure 5.2.

We can now save the extracted offset voltage  $V_{os}=19.992~\mu V$  that is required to bring the output voltage to  $V_{outq}=0.600~V$  and that will be used for the following .AC and .NOISE simulations.

## 5.3 Open-loop gain

After having checked the operating point information and making sure that the OTA output is not saturated by extracting the required offset voltage for bringing the output operating point to the desired value  $V_{outq} = 0.600 \ V$ , we can now perform the AC simulation.

From Figure 5.3, we see that the simulated gain-bandwidth product  $GBW = 1.141 \ MHz$  is about equal to the theoretical estimation 1.122 MHz and slightly above target 1.000 MHz. The simulated DC gain  $A_{dc} = 70.962 \ dB$  is way lower than the estimated DC gain 82.917 dB but still above the specifications 70 dB. This low DC gain is mainly due to the output conductance of  $M_{5b}$  which is very high despite the fact that the transistor length has been significantly increased and that the  $V_{DS}$  is

 


Figure 5.2: Zoom of the simulated large-signal input-output characteristic in the gain region.

 


Figure 5.3: Simulated gain response compared to theoretical estimation.

large enough. This is obviously due to the poor output conductance of the nMOS transistors and the low voltage constraint.

## 5.4 Input-referred noise

The simulated input-referred noise PSD is presented in Figure 5.4 and compared to the theoretical estimation.

 


Figure 5.4: Simulated input-referred noise PSD compared to theoretical estimation.

From Figure 5.4, we see that the simulated input-referred noise PSD is very close to the theoretical prediction. The simulated flicker noise is exactly equal to the theoretical estimation, while the simulated white noise is slightly higher. We can have a closer look at the contributions of the various transistors to the input-referred white noise PSD.

 


Figure 5.5: Breakdown of the contributions to the simulated input-referred white noise PSD.

The contributions of  $M_{1a}$ - $M_{1b}$ ,  $M_{2b}$ - $M_{2c}$ ,  $M_{4a}$ - $M_{4b}$  and  $M_{5a}$ - $M_{5b}$  to the input-referred white noise PSD are detailed in Figure 5.5 and compared to the theoretical white noise. Note that the contribution

of  $M_{3a}$ - $M_{3b}$  to the input-referred white noise PSD could not be extracted because it is very small. We can observe that the current mirror  $M_{2b}$ - $M_{2c}$  is contributing a bit more than the differential pair  $M_{1a}$ - $M_{1b}$ . This means that the simulated value of  $\eta_{th}$  is larger than the theoretical value  $\eta_{th} = 1.058$  given in Table 4.2. This is probably due to the fact that the simulated thermal noise excess factors of pMOS transistors shown in Table 5.7 are larger than the predicted values given in Table 4.2. As expected, the contributions of the cascode transistors  $M_{4a}$ - $M_{4b}$  is 30dB lower and that of  $M_{5a}$ - $M_{5b}$  is about 50 dB lower, conforming that they can indeed be neglected. The total simulated white noise is slightly higher than the theoretical estimation, which is acceptable. This results in an OTA thermal noise excess factor  $\gamma_{n,ota} = 3.066$  that is slightly larger than the predicted value  $\gamma_{n,ota} = 2.581$ . This is a rather high value of the thermal noise excess factor compared to other OTAs. Remember that this is due to the small gain  $G_{m1}/G_{m2} = 1.762$  because  $M_{2b}$ - $M_{2c}$  have a drain current 2.2 times larger than  $M_{1a}$ - $M_{1b}$ . Assuming that  $M_{1a}$ - $M_{1b}$  are biased in weak inversion and  $M_{2b}$ - $M_{2c}$  in strong inversion, the  $G_m$  ratio can then be written as

$$\frac{G_{m1}}{G_{m2}} \cong \frac{I_{b1}}{n_{0n} U_T} \cdot \frac{n_{0n} V_{P2}}{2 I_{b2}} = \frac{I_{b1}}{I_{b2}} \cdot \frac{V_{G2} - V_{T0n}}{2 n_{0n} U_T}.$$
 (5.1)

Now

$$\frac{I_{b2}}{I_{b1}} = \frac{I_{b1} + I_{b3}}{I_{b1}} = 1 + \alpha \tag{5.2}$$

and hence

$$\frac{G_{m1}}{G_{m2}} = \frac{1}{1+\alpha} \cdot \frac{V_{G2} - V_{T0n}}{2 \, n_{0n} \, U_T}.\tag{5.3}$$

The  $G_{m1}/G_{m2}$  gain can be increased by increasing the overdrive voltage  $V_{G2} - V_{T0n}$  or the inversion coefficient at the cost of a higher saturation voltage and hence a lower output voltage swing.

Figure 5.6 presents the breakdown of the contributions of the various transistors to the input-referred flicker noise. We see that it is dominated by the contributions of the current mirrors  $M_{2b}$ - $M_{2c}$  and  $M_{3a}$ - $M_{3b}$  which are larger than the contribution of the differential pair  $M_{1a}$ - $M_{1b}$ . This is consistent with the value of  $\eta_{fl} = 5.284$  given in Table 4.3.

The breakdown of the contributions of the various transistors to the total input-referred noise is presented in Figure 5.7. We can observe that the simulation is close to the theoretical estimation.

 


Figure 5.6: Breakdown of the contributions to the simulated input-referred flicker noise PSD.

 


Figure 5.7: Breakdown of the contributions to the simulated input-referred noise PSD.

### 5.5 Input common-mode voltage range

We can check the input common-mode voltage range by connecting the OTA as a voltage follower and sweeping the positive input. As shown in Figure 5.8, the output follows the input voltage from  $V_{in} = 0.22 V$  to about  $V_{in} = 1 V$  resulting in an input common-mode voltage range of about 0.78 V.

 


Figure 5.8: Simulated input common-mode voltage range.

## 5.6 Step-response

In this section we will check the step response of the OTA operating as a voltage follower as shown in Figure 5.9 with its output connected to the negative input and with the same load capacitance  $C_L = 1$  pF.

 


Figure 5.9: Schematic of the OTA connected as a voltage follower.

#### 5.6.1 Small-step

According to the input common-mode voltage range established above, we will set the input common-mode voltage to  $V_{ic} = 0.600~V$  to make sure that the OTA is in the high gain region. We start by imposing a small step  $\Delta V_{in} = 10~mV$  on top of a common mode voltage  $V_{ic} = 0.600~V$ . The simulation results are shown in Figure 5.10 where  $\Delta V_{in}(t) \triangleq V_{in+}(t) - V_{ic}$  and  $\Delta V_{out}(t) \triangleq V_{out}(t) - V_{outq}$  with  $V_{outq} \cong V_{ic}$  is the quiescent output voltage.  $\Delta V_{in}$  and  $\Delta V_{out}$  are compared to the response of a single pole circuit having a cut-off frequency equal to the GBW. From Figure 5.10, we see that the simulation result is very close to the first-order response.

 


Figure 5.10: Step response of the OTA connected as a voltage follower for a small input step.

#### 5.6.2 Large step

Since we now impose a larger step  $\Delta V_{in} = 300~mV$ , we need to lower the input common-mode voltage to  $V_{ic} = 400~mV$ , to make sure that after the step the OTA remains in the high gain region and correctly settles to the right voltage. The simulation results are shown in Figure 5.11 where  $\Delta V_{in}(t) \triangleq V_{in+}(t) - V_{ic}$  and  $\Delta V_{out}(t) \triangleq V_{out}(t) - V_{outq}$  with  $V_{outq} \cong V_{ic}$  is the quiescent output voltage.  $\Delta V_{in}$  and  $\Delta V_{out}$  are compared to the response of a single pole circuit having a cut-off frequency equal to the GBW. We now observe the effect of slew-rate which increases the settling time.

 


Figure 5.11: Step response of the OTA connected as a voltage follower for a large input step highlighting the slew-rate effect.

### 5.7 Current and power consumption

The total current consumption, ignoring the current drawn by  $M_{2a}$  and  $M_{7a}$ , is  $I_{tot} = 2I_{b2} = 1.1 \ \mu A$  and the power consumption is  $P = 1.320 \ \mu W$ .

Assuming the input differential pair  $M_{1a}$ - $M_{1b}$  is biased in deep weak inversion, the minimum bias current  $I_{b1,min}$  is directly related to the gain-bandwidth product GBW according to

$$I_{b1,min} \cong nU_T \cdot C_L \cdot \omega_u = nU_T \cdot C_L \cdot 2\pi \, GBW, \tag{5.4}$$

which is equal to 198 nA. The minimum total current consumption assuming  $\alpha \triangleq I_{b3}/I_{b1} = 1.2$  can then be estimated as  $I_{tot,min} \cong 2I_{b2,min} = 2(I_{b1,min} + I_{b3,min}) = 2I_{b1,min} (1 + \alpha) = 872 \ nA$ . The actual current consumption accounting for some margin taken on the GBW is therefore 26% higher than the minimum.

The current consumption of the folded cascode OTA is 2.2 times larger than that of the telescopic OTA for the same specifications.

#### i Note

Note that the telescopic OTA is the differential OTA that has the minimum power consumption for similar gain-bandwidth product, DC gain and phase margin specifications. Of course it has the smallest input and output voltage swings.

## 6 Conclusion

This notebook presented the detailed analysis, design and verification by simulation of the folded cascode OTA [1]. The analysis allowed to derive the design equations to achieve the target specifications. The OTA has been designed for specifications on the gain-bandwidth product and DC gain in the IHP SG13G2 130nm BiCMOS technology [2] using the inversion coefficient approach with the sEKV model and parameters [10] [11] [12]. The design has been validated by simulations with the ngspice simulator [3] using the PSP compact model [4] and the parameters provided by the open source IHP [2].

The simulations have shown that the target gain-bandwidth product GBW was achieved. The simulated DC gain is slightly less than the specification, despite the increase of the nMOS transistor length in the design phase. The estimated DC gain was  $A_{dc} \cong 82.9 \ dB$ , way above the simulated value of  $A_{dc} \cong 71.0 \ dB$  which is slightly above the  $A_{dc} = 70 \ dB$  specification. The noise simulations on the other hand match the theoretical values very well prooving the negligible contributions of the cascode transistors and showing that the corner frequency was slightly below the specification. Because of the high current in the current sources  $M_{2a}$ - $M_{2b}$ , it is difficult to minimize their contribution to the input-referred white noise resulting in a degraded thermal noise excess factor  $\gamma_{n,ota} = 3.066$ .

The folded cascode OTA is easier to design than the tlescopic OTA, because of the relaxed voltage constraints. It can reach higher DC gain and output voltage swing at the cost of more noise.

## References

- [1] T. C. Choi, R. T. Kaneshiro, R. W. Brodersen, P. R. Gray, W. B. Jett, and M. Wilcox, "High-frequency CMOS switched-capacitor filters for communications application," *IEEE Journal of Solid-State Circuits*, vol. 18, no. 6, pp. 652–664, 1983, doi: 10.1109/JSSC.1983.1052015.
- [2] IHP, "IHP SG13G2 Open Source PDK." https://github.com/IHP-GmbH/IHP-Open-PDK, 2025.
- [3] Holger Vogt, Giles Atkinson, Paolo Nenzi, "Ngspice User's Manual Version 43." https://ngspice.sourceforge.io/docs/ngspice-43-manual.pdf, 2024.
- [4] G.D.J. Smit, A.J. Scholten, D.B.M. Klaassen, O. Rozeau, S. Martinie, T. Poiroux and J.C. Barbé, "PSP 103.6 The PSP model is a joint development of CEA-Leti and NXP Semiconductors." https://www.cea.fr/cea-tech/leti/pspsupport/Documents/psp103p6\_summary.pdf, 2017.
- [5] F. Krummenacher, E. Vittoz, and M. Degrauwe, "Class AB CMOS amplifier micropower SC filters," *Electronics Letters*, vol. 17, no. 13, pp. 433–435, 1981.
- [6] M. G. Degrauwe, J. Rijmenants, E. A. Vittoz, and H. J. D. Man, "Adaptive biasing CMOS amplifiers," *IEEE Journal of Solid-State Circuits*, vol. 17, no. 3, pp. 522–528, 1982.
- [7] SemiMod GmbH, "Open VAF." https://openvaf.semimod.de/docs/getting-started/introduction/, 2025.
- [8] Dietmar Warning, "Verilog-A Models for Circuit Simulation." https://github.com/dwarning/VA-Models, 2024.
- [9] Agilent Technologies, "IC-CAP 2008, Nonlinear Device Models Volume 1." https://people.ece.ubc.ca/robertor/Links\_files/Files/ICCAP-2008-doc/pdf/icmdl.pdf, 2008.
- [10] C. C. Enz and E. A. Vittoz, Charge-Based MOS Transistor Modeling The EKV Model for Low-Power and RF IC Design, 1st ed. John Wiley, 2006.
- [11] C. Enz, F. Chicco, and A. Pezzotta, "Nanoscale MOSFET Modeling: Part 1: The Simplified EKV Model for the Design of Low-Power Analog Circuits," *IEEE Solid-State Circuits Magazine*, vol. 9, no. 3, pp. 26–35, 2017.
- [12] C. Enz, F. Chicco, and A. Pezzotta, "Nanoscale MOSFET Modeling: Part 2: Using the Inversion Coefficient as the Primary Design Parameter," *IEEE Solid-State Circuits Magazine*, vol. 9, no. 4, pp. 73–81, 2017.