

# **Cascode Gain Stage**

**For IHP 130nm Process (Version 1)**

Christian Enz ([christian.enz@epfl.ch](mailto:christian.enz@epfl.ch))

2025-05-04

# Table of contents

<b>1</b>	<b>Introduction</b>	<b>3</b>
<b>2</b>	<b>Analysis</b>	<b>4</b>
2.1	Small-signal analysis . . . . .	4
2.2	Noise analysis . . . . .	7
<b>3</b>	<b>Design</b>	<b>10</b>
3.1	Circuit . . . . .	10
3.2	Specifications . . . . .	10
3.3	Process . . . . .	11
3.4	Design procedure . . . . .	12
3.4.1	Sizing of $M_1$ . . . . .	12
3.4.2	Sizing the bias circuit . . . . .	14
3.4.3	Sizing of $M_2$ . . . . .	14
3.5	Summary . . . . .	14
3.5.1	Specifications . . . . .	14
3.5.2	Bias . . . . .	14
3.5.3	Transistor information . . . . .	15
<b>4</b>	<b>Theoretical estimations</b>	<b>16</b>
4.1	Transfer function . . . . .	16
4.2	Input-referred noise . . . . .	17
<b>5</b>	<b>Validation by simulation</b>	<b>19</b>
5.1	Operating point . . . . .	19
5.2	Small-signal transfer function . . . . .	22
5.3	Output resistance . . . . .	22
5.4	Input-referred noise . . . . .	24
<b>6</b>	<b>Conclusion</b>	<b>27</b>
	<b>References</b>	<b>28</b>

# 1 Introduction

This notebook presents the design of a cascode gain stage using the sEKV model and the inversion coefficient approach [1], [2], [3].

 


Figure 1.1: Schematic of the cascode gain stage.

The schematic of the cascode gain stage is shown in Figure 1.1. Let's start with the small-signal analysis.

## 2 Analysis

### 2.1 Small-signal analysis

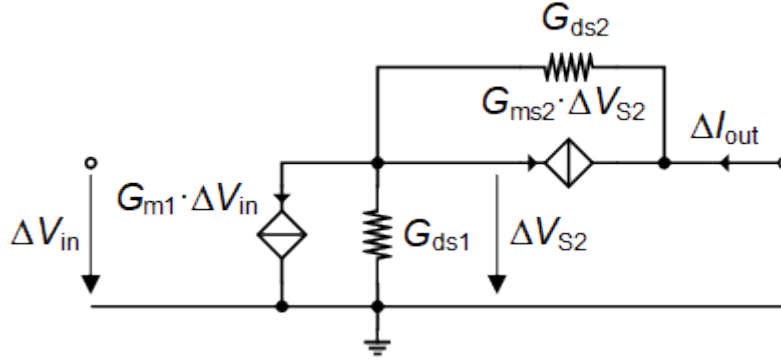


Figure 2.1: Small-signal schematic of the cascode stage for the calculation of the equivalent transconductance.

#### **i** Note

In the following analysis, the current source will be considered as ideal, i.e. zero output conductance. Of course, this current source is implemented by one or several transistors. In order not to degrade the overall output conductance and the DC gain, the current source should have an output conductance smaller than the cascode gain stage. This means that the current source should also be cascoded.

The small-signal schematic corresponding to Figure 1.1 for the derivation of the equivalent transconductance is given in Figure 2.1. Note that the output is short-circuited for calculating the short-circuit output current and the corresponding transconductance. The equivalent transconductance is given by

$$G_{meq} \triangleq \left. \frac{\Delta I_{out}}{\Delta V_{in}} \right|_{\Delta V_{out}=0} = \frac{G_{m1}(G_{ms2} + G_{ds2})}{G_{ms2} + G_{ds1} + G_{ds2}} \cong G_{m1}, \quad (2.1)$$

which shows that assuming  $G_{ms2} \gg G_{ds1}, G_{ds2}$ , the equivalent transconductance of the cascode stage is equal to the transconductance of the driver transistor  $M_1$ . This result is expected since the cascode transistor is a common gate stage which has a unity current gain so that the current coming from the driver transistor  $M_1$  is directly directed to the output.

The small-signal schematic for the calculation of the output conductance is shown in Figure 5.3. The output conductance is given by

$$G_{out} \triangleq \frac{\Delta I_{out}}{\Delta V_{out}} = \frac{G_{ds1}G_{ds2}}{G_{ms2} + G_{ds1} + G_{ds2}} \cong \frac{G_{ds1}}{G_{ms2}/G_{ds2}}, \quad (2.2)$$

which is equal to the output conductance of  $M_1$ ,  $G_{ds1}$ , divided by the voltage gain of the cascode  $G_{ms2}/G_{ds2}$ . This means that, at low-frequency, the output conductance of a single transistor can be reduced by adding a cascode stage at the cost of some voltage headroom to maintain  $M_2$  in saturation.

 


Figure 2.2: Small-signal schematic of the cascode stage for the calculation of the output conductance.

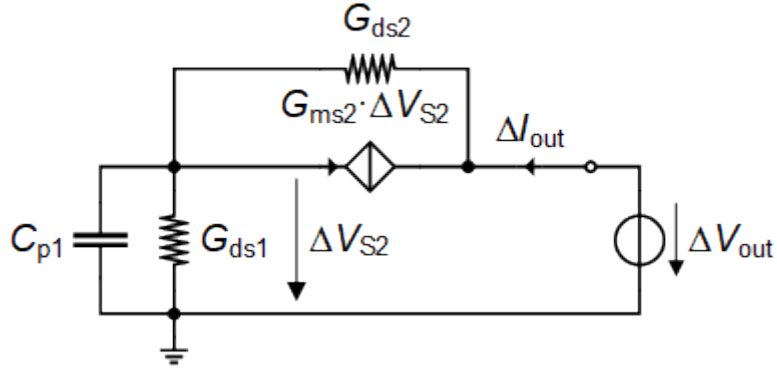


Figure 2.3: Small-signal schematic of the cascode stage for the calculation of the output conductance including the parasitic capacitance  $C_{p1}$ .

 


Figure 2.4: Effect of the parasitic capacitance  $C_{p1}$  on the output admittance  $Y_{out}$ .

The impact of the parasitic capacitance at node 1 on the output conductance can be investigated by adding the capacitance as shown in Figure 2.3. The output admittance then becomes

$$Y_{out} = G_{out} \cdot \frac{1 + s/\omega_z}{1 + s/\omega_p}, \quad (2.3)$$

where

$$G_{out} = \frac{G_{ds1} G_{ds2}}{G_{ms2} + G_{ds1} + G_{ds2}} \cong \frac{G_{ds1} G_{ds2}}{G_{ms2}}, \quad (2.4)$$

$$\omega_z = \frac{G_{ds1}}{C_{p1}}, \quad (2.5)$$

$$\omega_p = \frac{G_{ms2} + G_{ds1} + G_{ds2}}{C_{p1}} \cong \frac{G_{ms2}}{C_{p1}}. \quad (2.6)$$

The magnitude of  $Y_{out}$  versus frequency is sketched in Figure 2.4. For  $\omega \ll \omega_z \ll \omega_p$ ,  $Y_{out} \cong G_{out}$ . However for  $\omega_z \ll \omega_p \ll \omega$ , the output admittance becomes  $Y_{out} \cong G_{ds2}$ . We see that the cascode effect is lost. This can easily be understood since for  $\omega_p \ll \omega$ , the cascode node 1 is shortened to the ac ground and the voltage controlling the source of  $M_2$  is zero leaving the output conductance of  $M_2$  only.

 


Figure 2.5: Small-signal schematic for voltage gain calculation.

The transfer function can be calculated using the schematic shown in Figure 2.5 resulting in

$$A_v(s) = \frac{A_{dc}}{1 + s/\omega_c}, \quad (2.7)$$

with

$$A_{dc} = -\frac{G_{m1} (G_{ms2} + G_{ds2})}{G_{ds1} G_{ds2}} \cong -\frac{G_{m1} G_{ms2}}{G_{ds1} G_{ds2}}, \quad (2.8)$$

$$\omega_c = \frac{G_{ds1} G_{ds2}}{(G_{ms2} + G_{ds1} + G_{ds2}) C_L} \cong \frac{G_{ds1} G_{ds2}}{G_{ms2} C_L}. \quad (2.9)$$

.

The gain-bandwidth product is then given by

$$\omega_u = \frac{G_{m1} (G_{ms2} + G_{ds2})}{(G_{ms2} + G_{ds1} + G_{ds2}) C_L} \cong \frac{G_{m1}}{C_L}, \quad (2.10)$$

which, as expected, is equal to the ratio of the cascode equivalent transconductance  $G_{m1}$  to the load capacitance  $C_L$ .

 


Figure 2.6: Small-signal schematic of the cascode stage for the noise calculation.

## 2.2 Noise analysis

To calculate the output noise power spectral density (PSD) we can use the schematic shown in Figure 2.6. The output noise current is then given by

$$I_{nout} = \frac{G_{ms2} + G_{ds2}}{G_{ms2} + G_{ds1} + G_{ds2}} \cdot I_{n1} + \frac{G_{ds1}}{G_{ms2} + G_{ds1} + G_{ds2}} \cdot I_{n2} \cong I_{n1} + \frac{I_{n2}}{G_{ms2}/G_{ds1}}, \quad (2.11)$$

for  $G_{ms2} \gg G_{ds1}, G_{ds2}$ . We see that the contribution to the output noise current of the cascode stage is actually divided by  $G_{ms2}/G_{ds1}$ . Provided that this gain can be made sufficiently large and that both transistors have the same noise, the noise of the cascode stage can be made negligible compared to the noise due to  $M_1$ . Ultimately if  $G_{ds1} = 0$ , the noise current  $I_{n2}$  circulates in the cascode transistor  $M_2$  ( $G_{ms2}$  in the small-signal schematic) and hence does not reach the output.

The output noise conductance is then given by

$$G_{nout}(f) \cong G_{n1}(f) + \left( \frac{G_{ds1}}{G_{ms2}} \right)^2 G_{n2}(f) \quad (2.12)$$

where the noise conductances are given by

$$G_{ni}(f) = \gamma_{ni} \cdot G_{mi} + \frac{\rho_n}{f W_i L_i} \cdot G_{mi}^2 \quad \text{for } i = 1, 2. \quad (2.13)$$

The input-referred noise is obtained by dividing  $G_{nout}$  by  $G_{meq}^2$ , resulting in

$$R_{nin} = \frac{G_{nout}(f)}{G_{meq}}. \quad (2.14)$$

It can be decomposed into the thermal and flicker noise components according to

$$R_{nin} = R_{nt} + R_{nf}(f) \quad (2.15)$$

where  $R_{nt}$  is the total input-referred thermal noise

$$R_{nt} \cong \frac{\gamma_{n1}}{G_{m1}} + \left( \frac{G_{ds1}}{G_{m1}} \right)^2 \frac{\delta_{n2}}{G_{ms2}} = \frac{\gamma_{n1}}{G_{m1}} (1 + \eta_{th}), \quad (2.16)$$

where

$$\eta_{th} = \frac{G_{ds1}^2}{G_{m1} G_{ms2}} \frac{\delta_{n2}}{\gamma_{n1}} \ll 1 \quad (2.17)$$

represents the contribution to the input-referred thermal noise of the cascode transistor  $M_2$  relative to that of the driver transistor  $M_1$ . Since for long-channel transistors  $\gamma_{n1}$  and  $\delta_{n2}$  are of the same order of magnitude and since  $G_{m1}G_{ms2} \gg G_{ds1}^2$  then  $\eta_{th} \ll 1$ . This means that the contribution of the cascode transistor to the input-referred thermal noise is negligible.

$R_{nf}(f)$  is the input-referred 1/f noise

$$R_{nf}(f) \cong \frac{\rho_n}{f W_1 L_1} + \left( \frac{G_{ds1}}{G_{m1}} \right)^2 \frac{\rho_n}{n_2^2 f W_2 L_2} = \frac{\rho_n}{f W_1 L_1} \cdot (1 + \eta_{fl}), \quad (2.18)$$

where

$$\eta_{fl} = \left( \frac{G_{ds1}}{n_2 G_{m1}} \right)^2 \frac{W_1 L_1}{W_2 L_2} \quad (2.19)$$

represents the contribution to the input-referred flicker noise of the cascode transistor  $M_2$  relative to the driver transistor  $M_1$ . If  $M_1$  and  $M_2$  have about the same area, then  $\eta_{fl} \ll 1$ , meaning that the contribution of the cascode transistor to the input-referred flicker noise is negligible.

The  $\gamma_n$  noise factor of the cascode stage is given by

$$\gamma_{cas} \triangleq G_{meq} \cdot R_{nt} = G_{m1} \cdot R_{nt} = \gamma_{n1} \cdot (1 + \eta_{th}) \cong \gamma_{n1}, \quad (2.20)$$

since  $G_{m1}G_{ms2} \gg G_{ds1}^2$ . The contribution of the cascode transistor to the overall noise excess factor is therefore negligible. The same remark holds for the 1/f noise. Indeed, assuming  $M_1$  and  $M_2$  have the same area and  $G_{m1}/G_{ds1} \gg 1$ , (2.18) simplifies to

$$R_{nf}(f) \cong \frac{\rho_n}{f W_1 L_1}, \quad (2.21)$$

which corresponds to the contribution of  $M_1$  only.

 


Figure 2.7: Small-signal schematic of the cascode stage for the calculation of the output noise including the effect of the parasitic capacitance  $C_{p1}$

Similarly, the impact of the parasitic capacitance on the noise can be calculated from Figure 2.7. The output noise conductance is then given by

$$G_{nout} = |H_{n1}(\omega)|^2 \cdot G_{n1} + |H_{n2}(\omega)|^2 \cdot G_{n2}, \quad (2.22)$$

where

$$H_{n1}(s) = \frac{G_{ms2} + G_{ds2}}{G_{ms2} + G_{ds1} + G_{ds2}} \cdot \frac{1}{1 + s/\omega_p} \cong \frac{1}{1 + s/\omega_p} \quad (2.23)$$

$$H_{n2}(s) = \frac{G_{ds1}}{G_{ms2} + G_{ds1} + G_{ds2}} \cdot \frac{1 + s/\omega_z}{1 + s/\omega_p} \cong \frac{G_{ds1}}{G_{ms2}} \cdot \frac{1 + s/\omega_z}{1 + s/\omega_p}. \quad (2.24)$$

The magnitude of  $H_{n1}$  and  $H_{n2}$  versus frequency are sketched in Figure 2.8. For  $\omega \ll \omega_z \ll \omega_p$ ,  $H_{n1} \cong 1$  and  $H_{n2} \cong G_{ds1}/G_{ms2}$  which is the result obtained above. However, for  $\omega_z \ll \omega_p \ll \omega$ ,  $H_{n1} \cong \omega_p/s$



 


Figure 2.8: Noise transfer functions  $H_{n1}$  and  $H_{n2}$  versus frequency.

and  $H_{n2} \cong 1$ . We see that the cascode effect is lost since the noise of  $M_2$  is no more divided by the cascode gain  $G_{ms2}/G_{ds1}$  but is entirely transferred to the output.

As a conclusion, adding a cascode stage reduces the output conductance without penalty on the noise, but at the cost of a slight voltage overhead for maintaining  $M_2$  in saturation. This is only true for  $\omega < \omega_z = G_{ds1}/C_{p1}$ . For frequencies  $\omega \gg \omega_p = G_{ms2}/C_{p1}$  the cascode effect is lost. Note that in order to maximize  $G_{ms2}$  at a given current and minimize its saturation voltage,  $M_2$  should be biased in weak inversion.

We now will use the above equations to design the cascode gain stage.

## 3 Design

### 3.1 Circuit

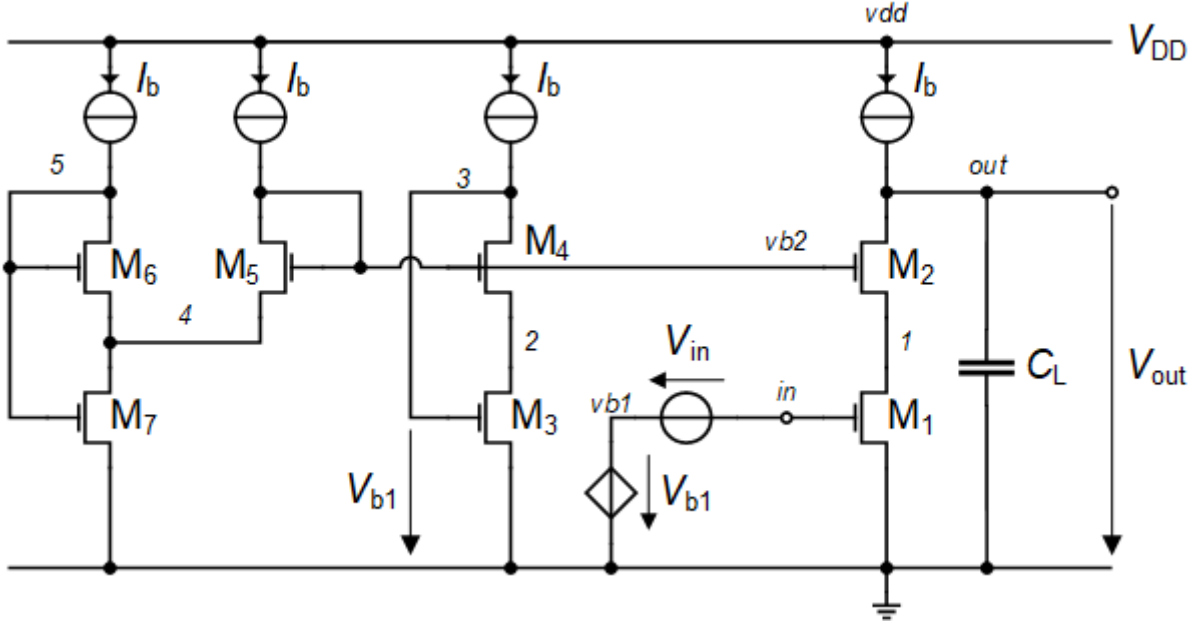


Figure 3.1: Cascode gain stage including the bias circuit.

The schematic of the cascode gain stage is shown in Figure 3.1. We have included the bias circuit made of transistors  $M_3$  to  $M_7$ . Transistors  $M_3$  and  $M_4$  are added to correctly set the gate bias voltage of  $M_1$  for the bias current  $I_b$  for the simulation.  $M_3$  and  $M_4$  are made identical to  $M_1$  and  $M_2$ , respectively. They are sharing the same cascode bias voltage  $V_{b2}$  generated by transistors  $M_5$ ,  $M_6$  and  $M_7$ . Assuming that transistors  $M_5$ ,  $M_6$  and  $M_7$  are all biased in weak inversion, it can be shown that the drain voltage  $V_{D1}$  (voltage at node 1), is given by

$$V_{D1} = U_T \cdot \ln \left[ \frac{\beta_2}{\beta_5} \left( 1 + 2 \frac{\beta_6}{\beta_7} \right) \right], \quad (3.1)$$

where

$$\beta = \frac{I_{spec}}{2nU_T^2} = \mu C_{ox} \frac{W}{L}. \quad (3.2)$$

The bias voltage  $V_{D1}$  should be at least  $4U_T$ . If we make  $M_5$  identical to  $M_2$  and  $M_4$ , then  $\beta_2/\beta_5 = 1$ . To get  $V_{D1} = 4U_T$  would require  $\beta_6/\beta_7 \cong 54$  which is prohibitive. We therefore need to take advantage of the additional degree of freedom choosing  $\beta_2 > \beta_5$ . For example if we take  $\beta_2/\beta_5 = \beta_6/\beta_7 = 5$  we get  $V_{D1} \cong 4U_T$ .

### 3.2 Specifications

We will design the cascode gain stage for the specifications given in Table 3.1, namely a given gain-bandwidth product  $GBW$  and DC gain  $A_{dc}$ . Note that, contrary to the common-source optimization,

in this design, increasing the width of  $M_1$  does not increase the load capacitance but increases the parasitic capacitance  $C_{p1}$  at the cascode node.

Table 3.1: Specifications.

Specification	Symbol	Value	Unit
Minimum DC gain	$A_{dc}$	100	-
Minimum DC gain	$A_{dc}$	40	$dB$
Minimum gain-bandwidth product	$GBW$	1	$MHz$
Load capacitance	$C_L$	1	$pF$

### 3.3 Process

We will design the cascode gain stage for the open source IHP 13G2 BiCMOS process [4]. The physical parameters are given in Table 3.2, the global process parameters in Table 3.3 and finally the MOSFET parameters in Table 3.4.



#### Warning

The matching parameters for IHP 130nm are unknown. We will use those from a generic 180nm technology.

Table 3.2: Physical parameters

Parameter	Value	Unit
$T$	300	$K$
$U_T$	25.865	$mV$

Table 3.3: Process parameters.

Parameter	Value	Unit	Comment
$t_{ox}$	2.24	$nm$	SiO <sub>2</sub> oxide thickness
$C_{ox}$	15.413	$\frac{fF}{\mu m^2}$	Oxide capacitance per unit area
$V_{DD}$	1.2	$V$	Nominal supply voltage
$L_{min}$	130	$nm$	Minimum drawn gate length
$W_{min}$	150	$nm$	Minimum drawn gate width
$z_1$	340	$nm$	Minimum outer diffusion width
$z_2$	389	$nm$	Minimum diffusion width between two fingers

Table 3.4: Transistors parameters.

	Parameter	nMOS	pMOS	Unit
Length and width correction parameters for current				
	$DL$	59	51	$nm$
	$DW$	-20	30	$nm$
Length and width correction for intrinsic and overlap capacitances				
	$DLCV$	93	146	$nm$
	$DWCV$	-10	15	$nm$

Table 3.4: Transistors parameters.

	Parameter	nMOS	pMOS	Unit
Length and width correction parameter for fringing capacitances				
	$DLGCV$	34	96	$nm$
	$DWGCV$	10	-15	$nm$
Long-channel sEKV parameters parameters				
	$n$	1.22	1.23	-
	$I_{spec\Box}$	708	245	$nA$
	$V_{T0}$	246	365	$mV$
Short-channel sEKV parameters parameters				
	$L_{sat}$	7.1	24.9	$nm$
	$\lambda$	1.375	6.078	$\frac{V}{\mu m}$
Junction capacitances parameters				
	$C_J$	0.976	0.863	$\frac{fF}{\mu m^2}$
	$C_{JSWSTI}$	0.025	0.032	$\frac{fF}{\mu m}$
	$C_{JSWGAT}$	0.03	0.027	$\frac{fF}{\mu m}$
Overlap capacitances parameters				
	$C_{GSo}$	0.453	0.443	$\frac{fF}{\mu m}$
	$C_{GDo}$	0.453	0.443	$\frac{fF}{\mu m}$
	$C_{GBo}$	0	0.022	$\frac{fF}{\mu m}$
Fringing capacitances parameters				
	$C_{GSf}$	0.2	0.1	$\frac{fF}{\mu m}$
	$C_{GDf}$	0.2	0.1	$\frac{fF}{\mu m}$
Flicker noise parameters				
	$K_F$	2.208e-24	1.2e-23	$VAs$
	$AF$	1	1	-
	$\rho$	0.008642	0.04697	$\frac{Vm^2}{As}$
Matching parameters				
	$A_{VT}$	5	5	$mV \cdot \mu m$
	$A_\beta$	1	1	$\% \cdot \mu m$

As shown in Figure 3.2, it is worth noting that the threshold voltage in saturation is strongly dependent on the gate length [5]. From Figure 3.2, we see that the threshold voltage for a long-channel transistor with  $V_{SB} = 0$  is as low as  $V_{T0} \cong 50 mV$ . It then increases to about  $V_{T0} \cong 250 mV$  for a short-channel transistor. This threshold voltage change (about 200 mV) can have an important impact on the bias voltages, such as the voltages generated by the bias circuit shown in Figure 3.1.

## 3.4 Design procedure

### 3.4.1 Sizing of $M_1$

$M_1$  is biased in weak inversion in order to maximize the current efficiency and is sized according to the specification on the GBW and the load capacitance according to

$$GBW = \frac{G_{m1}}{2\pi C_L}. \quad (3.3)$$

The gate transconductance of  $M_1$   $G_{m1}$  in deep weak inversion is given by

$$G_{m1} = \frac{I_b}{nU_T}. \quad (3.4)$$

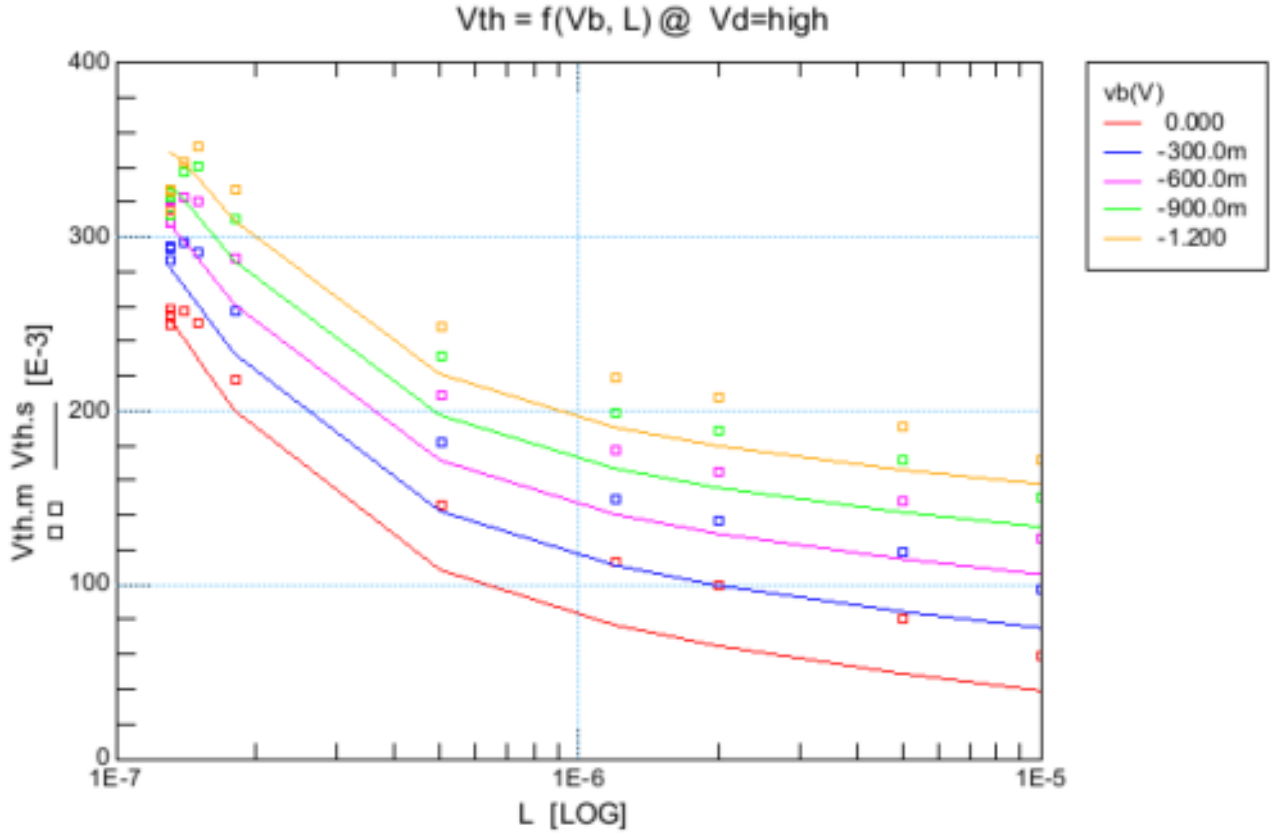


Figure 3.2: Threshold voltage of nMOS transistor in saturation versus gate length  $L$ .

The bias current  $I_b$  must satisfy the following inequality

$$I_b \geq 2\pi n_{0n} U_T C_L GBW_{min}, \quad (3.5)$$

which for the given specifications gives  $I_{b,min} = 198 \text{ nA}$ .

To have some margin to account for the additional parasitic capacitance at the output that add to the load capacitance  $C_L$ , we set  $I_b = 250 \text{ nA}$  and the inversion coefficient of  $M_1$  to  $IC_1 = 0.1$ . The transconductance can be calculated from the  $G_m/I_D$  function as

$$G_{m1} = \frac{I_b}{n_{0n} U_T} \cdot gmsid(IC_1) = 7.258 \frac{\mu A}{V}.$$

This leads to a gain-bandwidth product

$$GBW = \frac{G_{m1}}{2\pi C_L} = 1.2 \text{ MHz},$$

which is slightly higher than the target specification offering some margin.

Knowing the drain current  $I_{D1}$  and the inversion coefficient, we can calculate the  $W/L$  aspect ratio for  $M_1$  as

$$\frac{W_1}{L_1} = \frac{I_b}{I_{spec,n} IC_1} = 3.5.$$

To choose the length of  $M_1$ , we can split the gain equally between the driver transistor  $A_{v1} = G_{m1}/G_{ds1}$  and the cascode transistor  $A_{v2} = G_{ms2}/G_{ds2}$ . This leads to  $A_{v1} = A_{v2} = 10$  giving the desired overall gain of  $A_{dc} = 40 \text{ dB}$ . We can then deduce the transistor length and width as

$$L_1 = 250 \text{ nm and}$$

$$W_1 = 880 \text{ nm}.$$

Before sizing  $M_2$  we need to size  $M_5$ .

### 3.4.2 Sizing the bias circuit

Since we need to bias  $M_2$ ,  $M_4$  and  $M_5$  in weak inversion we need to make sure that  $M_2$  and  $M_4$  remain in weak inversion despite they are much wider than  $M_5$  and biased with the same current  $I_b$ . For this reason we start sizing  $M_5$  first. Since we know the drain current of  $M_5$ , if we choose its inversion coefficient we get the  $W/L$ . Let's choose  $IC_5 = 0.1$  for which we get  $W/L = 3.530$ . As mentioned above, we need to be careful choosing the length of  $M_5$  because of the strong dependence of the threshold voltage to the transistor length. Since the bias circuit is based on the assumption that all the transistors have the same threshold voltage, it is safer to choose the same length for all transistors. We can choose  $L_1$  since we already have chosen it. Therefore  $L_7 = L_6 = L_5 = L_4 = L_3 = L_2 = L_1 = 250 \text{ nm}$ . This leads to  $W_5 = 880 \text{ nm}$  and  $L_5 = 250 \text{ nm}$ .

Note that choosing  $L_2 = L_1$  leads to  $G_{ds2} \cong G_{ds1}$  since  $M_1$  and  $M_2$  carry the same current. The DC gain of the cascode transistor  $G_{ms2}/G_{ds2}$  should be slightly larger than the DC gain of the driver transistor  $G_{m1}/G_{ds1} = 10$ , because  $G_{ms2} > G_{m1}$ . The DC gain should therefore be achieved.

Since  $M_7$  carries twice the current of  $M_1$ , if we want  $M_7$  to have the same inversion coefficient than  $M_1$ , we need to choose  $W_7 = 2W_1 = 1.76 \text{ }\mu\text{m}$ . The width of  $M_6$  needs to be 5 times larger than  $W_7$  leading to  $W_6 = 5W_7 = 8.80 \text{ }\mu\text{m}$ .

Finally  $M_3$  is taken identical to  $M_1$  resulting in  $W_3 = W_1 = 0.88 \text{ }\mu\text{m}$  and  $L_3 = 250 \text{ nm}$ .

### 3.4.3 Sizing of $M_2$

We can now finalize the design by sizing  $M_2$ . In order to save voltage headroom we need to bias  $M_2$  in weak inversion. This is done by choosing  $W_2$  to be 5 times  $W_5$ , leading to  $W_2 = 4.40 \text{ }\mu\text{m}$  with  $L_2 = 250 \text{ nm}$ . With these dimensions, the inversion coefficient of  $M_2$  is 5 times smaller than that of  $M_5$ ,  $IC_2 = 0.020$ , which is making sure that  $M_2$  is biased in weak inversion. We can now check the DC gain. The source transconductance and output conductance of  $M_2$  are equal to  $G_{ms2} = 9.479 \text{ }\mu\text{A/V}$  and  $G_{ds2} = 727.273 \text{ nA/V}$ . This leads to a cascode voltage gain of  $A_{v2} = 13.03$  and an overall gain  $A_{dc} = 42.30 \text{ dB}$  which, as expected, is slightly higher than the specs.

The sizing procedure is now finished and is summarized in the next section.

## 3.5 Summary

### 3.5.1 Specifications

The specifications are recalled in Table 3.5.

Table 3.5: Specifications.

Specification	Symbol	Value	Unit
Minimum DC gain	$A_{dc}$	40	$\text{dB}$
Minimum gain-bandwidth product	$GBW$	1	$\text{MHz}$
Load capacitance	$C_L$	1	$\text{pF}$

### 3.5.2 Bias

The bias information are summarized in Table 3.6.

Table 3.6: Bias information.

Bias voltage or current	Symbol	Value	Unit
Supply voltage	$V_{DD}$	1.2	V
Bias current	$I_b$	250	nA

### 3.5.3 Transistor information

The transistor sizes and bias information are summarized in Table 3.7 and Table 3.8, respectively. Table 3.9 gives the small-signal and thermal noise parameters. An Excel table is generated with more information (e.g. all the parasitic capacitances).

Table 3.7: Transistor size information.

Transistor	$W$ [ $\mu m$ ]	$L$ [ $\mu m$ ]	$W_{eff}$ [ $\mu m$ ]	$L_{eff}$ [ $\mu m$ ]	$W/L$	$AD$ [ $\mu m^2$ ]	$PD$ [ $\mu m$ ]
M1	0.88	0.25	0.900	0.191	4.708	0.299	2.440
M2	4.40	0.25	4.420	0.191	23.123	1.496	9.480
M3	0.88	0.25	0.900	0.191	4.708	0.299	2.440
M4	4.40	0.25	4.420	0.191	23.123	1.496	9.480
M5	0.88	0.25	0.900	0.191	4.708	0.299	2.440
M6	8.80	0.25	8.820	0.191	46.141	2.992	18.280
M7	1.76	0.25	1.780	0.191	9.312	0.598	4.200

Table 3.8: Transistor bias information.

Transistor	$I_D$ [nA]	$I_{spec}$ [nA]	$IC$	$V_P - V_S$ [mV]	$V_G - V_{T0}$ [mV]	$V_{DSsat}$ [mV]
M1	250	3335	0.075	-65	-53	104
M2	250	16378	0.015	-108	-88	104
M3	250	3335	0.075	-65	-53	104
M4	250	16378	0.015	-108	-88	104
M5	250	3335	0.075	-65	-53	104
M6	250	32682	0.008	-126	-103	104
M7	500	6596	0.076	-65	-53	104

Table 3.9: Transistor small-signal and thermal noise parameters.

Transistor	$G_{spec}$ [ $\mu A/V$ ]	$G_{ms}$ [ $\mu A/V$ ]	$G_m$ [ $\mu A/V$ ]	$G_{ds}$ [nA/V]	$\gamma_n$
M1	128.933	9.033	7.404	727.273	0.623
M2	633.206	9.522	7.805	727.273	0.613
M3	128.933	9.033	7.404	727.273	0.623
M4	633.206	9.522	7.805	727.273	0.613
M5	128.933	9.033	7.404	727.273	0.623
M6	1263.547	9.593	7.863	727.273	0.612
M7	255.002	18.053	14.798	1454.545	0.623

## 4 Theoretical estimations

We can now check the transfer function and the input-referred noise PSD.

### 4.1 Transfer function

The parameters that are required to evaluate the transfer function are calculated in Table 4.1.

Table 4.1: Small-signal parameters required to calculate the transfer function.

Symbol	Theoretical Value	Unit
$A_{dc}$	43	$dB$
$G_{m1}$	7.404	$\mu A/V$
$G_{ms2}$	9.522	$\mu A/V$
$f_c$	7.669	$kHz$
$GBW$	1.1	$MHz$

Using the values given in Table 4.1, we can now plot the transfer function which is plotted in Figure 4.1.

### 4.2 Input-referred noise

We can now compute all the parameters needed for the calculation of the OTA thermal noise excess factor and its input-referred thermal noise resistance. They are given in Table 4.2.

#### Warning

In order to check the effect of the cascode on the noise, we will ignore the noise contribution of the bias circuit. Of course in reality the bias circuit will also contribute to the output noise.

Table 4.2: Thermal noise parameters.

Symbol	Theoretical Value	Unit
$G_{m1}$	7.404	$\mu A/V$
$G_{ms2}$	9.522	$\mu A/V$
$G_{ds1}$	0.727	$\mu A/V$
$G_{m1} G_{ms2}/G_{ds1}^2$	133.295	-
$\gamma_{n1}$	0.623	-
$\delta_{n2}$	0.502	-
$\eta_{th}$	0.006048	-
$R_{nt}$	84.696	$k\Omega$
$\gamma_{cas}$	0.627	-
$\sqrt{S_{ninth}}$	37.469	$nV/\sqrt{Hz}$



Table 4.2: Thermal noise parameters.

Symbol	Theoretical Value	Unit
$10 \cdot \log(S_{ninth})$	-148.527	$dBv/\sqrt{Hz}$

Table 4.3: Flicker noise parameters.

Symbol	Theoretical Value	Unit
$(n_2 G_{m1}/G_{ds1})^2$	154.3	-
$\frac{W_1 \cdot L_1}{W_2 \cdot L_2}$	0.2	-
$\eta_{fl}$	0.001	-
$\sqrt{S_{ninfl}(1 Hz)}$	28.9	$\mu V/\sqrt{Hz}$
$10 \cdot \log(S_{ninfl}(1 Hz))$	-90.8	$dBv/\sqrt{Hz}$
$f_k$	929	$kHz$

We can plot the input-referred noise PSD which is shown in Figure 4.2.

 


Figure 4.1: Theoretical transfer function.

 


Figure 4.2: Theoretical input-referred noise PSD.

## 5 Validation by simulation

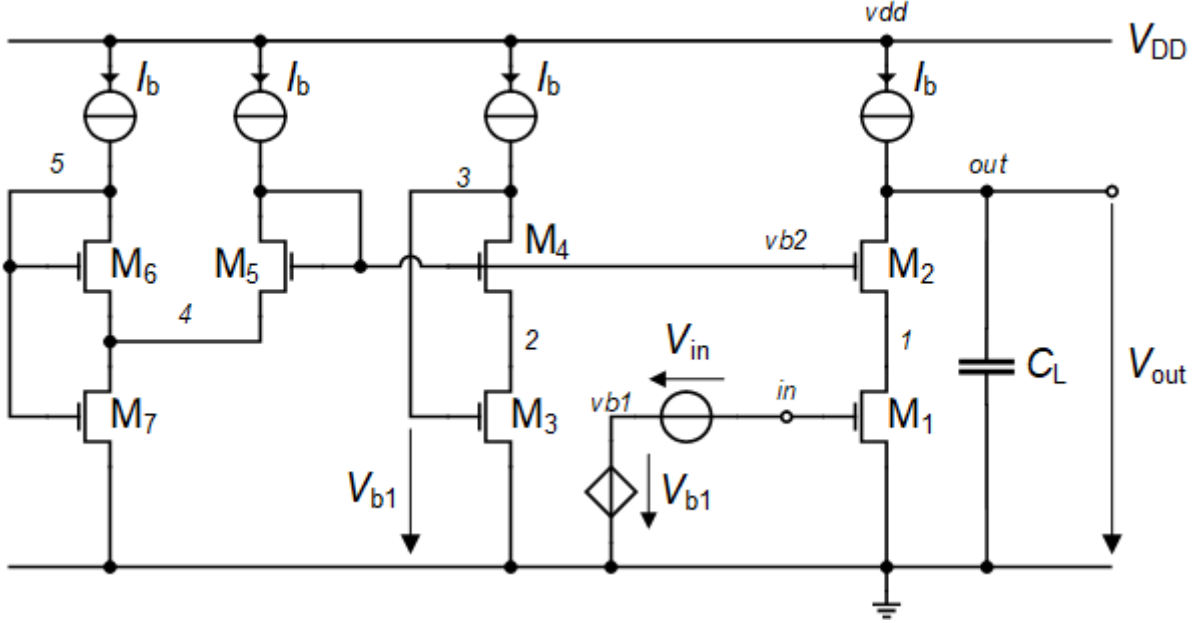


Figure 5.1: Schematic of the cascode gain stage used for simulation.

The above design can be verified using ngspice simulations. We will use the circuit shown in Figure 5.1 to run the simulations. Note that the bias voltage  $V_{b1}$  is generated by the additional current branch with  $M_3$  and  $M_4$ . In this way we ensure that the DC gate voltage of  $M_1$  actually corresponds to its drain current. The bias voltage  $V_{b2}$  is generated by transistors  $M_5$ ,  $M_6$  and  $M_7$ .

### **i** Note

The simulations are performed with the PSP 103.6 compact model [6]. For ngspice, we use the Verilog-A implementation given in the IHP package [4] and compiled the OSDI file with OpneVAF [7] to run with ngspice [8]. In addition to the PSP user manual [6] a documentation of PSP and other MOSFET compact models and their parameter extraction can be found in [9].

We start checking the transistors operating point in the next section.

### 5.1 Operating point

Before running the AC and NOISE simulations, we first need to check the quiescent voltages and currents and the operating points of all transistors by running an .OP simulation. The node voltages are extracted from the .ic file and presented in Table 5.1. The transistor drain current and voltages are presented in Table 5.2. The small-signal parameters are given in Table 5.3 and the noise PSD are given in Table 5.4.

Table 5.1: Cascode gain stage node voltages.

Node	Voltage
vdd	1.2
in	0.302368
out	0.302368
vb1	0.302368
vb2	0.409582
1	0.159909
2	0.159909
3	0.302368
4	0.103188
5	0.302163

Table 5.2: PSP operating point information extracted from ngspice .op file for each transistor.

Transistor	$I_D$ [nA]	$V_{GS}$ [mV]	$V_{DS}$ [mV]	$V_{SB}$ [mV]	$V_{GS} - V_T$ [mV]	$V_{Dsat}$ [mV]
M1	250	302	160	0	-49	116
M2	250	250	142	160	-104	115
M3	250	302	160	0	-49	116
M4	250	250	142	160	-104	115
M5	250	306	306	103	-58	116
M6	250	199	199	103	-131	114
M7	500	302	103	0	-47	117

Table 5.3: PSP small-signal operating point information extracted from ngspice .op file for each transistor.

Transistor	$G_m$ [ $\mu A/V$ ]	$G_{mb}$ [ $\mu A/V$ ]	$G_{ds}$ [nA/V]
M1	6.729	0.971	520.208
M2	7.408	0.954	638.083
M3	6.729	0.971	520.208
M4	7.408	0.954	638.083
M5	6.823	0.899	429.712
M6	7.501	0.959	536.693
M7	13.424	1.933	1418.369

Table 5.4: PSP noise operating point information extracted from ngspice .op file for each transistor.

Transistor	$S_{ID,th}$ [ $A^2/Hz$ ]	$S_{ID,fl}$ at 1Hz [ $A^2/Hz$ ]
M1	7.304e-26	2.778e-20
M2	7.676e-26	6.483e-21
M3	7.304e-26	2.778e-20
M4	7.676e-26	6.483e-21
M5	7.179e-26	2.233e-20
M6	7.523e-26	2.993e-21
M7	1.549e-25	6.015e-20

Table 5.5: sEKV parameters calculated from the values extracted from the simulation.

Transistor	$W_{eff} [\mu m]$	$L_{eff} [\mu m]$	$W_{eff}/L_{eff}$	$I_{spec} [\mu A]$	$IC$
M1	0.900	0.191	4.708	3.335	0.075
M2	4.420	0.191	23.123	16.378	0.015
M3	0.900	0.191	4.708	3.335	0.075
M4	4.420	0.191	23.123	16.378	0.015
M5	0.900	0.191	4.708	3.335	0.075
M6	8.820	0.191	46.141	32.682	0.008
M7	1.780	0.191	9.312	6.596	0.076

Table 5.6: sEKV small-signal parameters calculated from the values extracted from the simulation.

Transistor	$G_{spec} [\mu A/V]$	$n$	$G_m [\mu A/V]$	$G_{ms} [\mu A/V]$	$G_{ds} [nA/V]$
M1	128.933	1.144	6.729	7.700	520.208
M2	633.206	1.129	7.408	8.362	638.083
M3	128.933	1.144	6.729	7.700	520.208
M4	633.206	1.129	7.408	8.362	638.083
M5	128.933	1.132	6.823	7.721	429.712
M6	1263.547	1.128	7.501	8.460	536.693
M7	255.002	1.144	13.424	15.357	1418.369

Table 5.7: sEKV noise parameters calculated from the values extracted from the simulation.

Transistor	$\sqrt{S_{nin,th}} [nV/\sqrt{Hz}]$	$R_{nin,th} [k\Omega]$	$\gamma_n [-]$	$\sqrt{S_{nin,fl}} [nV/\sqrt{Hz}]$
M1	40.166	97.329	0.655	24768.869
M2	37.398	84.377	0.625	10868.814
M3	40.166	97.329	0.655	24768.870
M4	37.398	84.377	0.625	10868.820
M5	39.272	93.045	0.635	21900.429
M6	36.567	80.665	0.605	7294.033
M7	29.319	51.860	0.696	18270.585

Table 5.8: Bias voltages and operating regions of each transistor.

Trans.	Type	$V_G [V]$	$V_S [V]$	$V_D [V]$	$V_{DS} [mV]$	$V_{DSsat} [mV]$	Reg.	Sat.
M1	n	0.302	0.000	0.160	160	116	WI	sat
M2	n	0.410	0.160	0.302	142	115	WI	sat
M3	n	0.302	0.000	0.160	160	116	WI	sat
M4	n	0.410	0.160	0.302	142	115	WI	sat
M5	n	0.410	0.103	0.410	306	116	WI	sat
M6	n	0.302	0.103	0.302	199	114	WI	sat
M7	n	0.302	0.000	0.103	103	117	WI	lin

From Table 5.1, we observe that the drain voltage of M<sub>1</sub> (voltage at node 1) is  $V_{D1} = V(1) = 160 \text{ mV}$  which is slightly larger than  $4U_T = 104 \text{ mV}$ . This comes from the fact that transistor M<sub>5</sub> is not biased deep in weak inversion but with an inversion coefficient  $IC_5 = 0.075$  which makes its  $V_{GS}$  voltage larger moving the voltage at node 1 a bit higher.

The  $V_{DS}$  voltages of Table 5.2 are all larger than the  $V_{Dsat}$  voltages, confirming that all the transistors are biased in saturation. This is also confirmed in Table 5.8.

Comparing to the theoretical values of Table 3.9, we see that the simulated transconductance values are slightly smaller than the theoretical values, while the simulated output conductances are smaller than the theoretical values.

## 5.2 Small-signal transfer function

After having checked the operating point and making sure that all transistors are biased in saturation, we can now perform the AC simulation. The simulation results are compared to the theoretical estimations in Figure 5.2. The simulated  $GBW$  is slightly smaller than the theoretical value but remains on target. The simulated DC gain is larger than the theoretical estimation.

 


Figure 5.2: Simulated gain response compared to theoretical estimation.

## 5.3 Output resistance

We can check that the cascode significantly reduces the output conductance (increases the output resistance). In order to do this we add an AC current source at the output with zero DC value as shown in Figure 5.3. This AC current source will not change the quiescent output voltage but will inject a small-signal current at the output. Measuring the output voltage we can then deduce the output admittance or impedance.

The result of the simulation is presented in Figure 5.4 where the simulated small-signal output impedance is plotted versus frequency and compared to  $R_{ds1} = 1/G_{ds1}$ ,  $R_{ds2} = 1/G_{ds2}$  and the

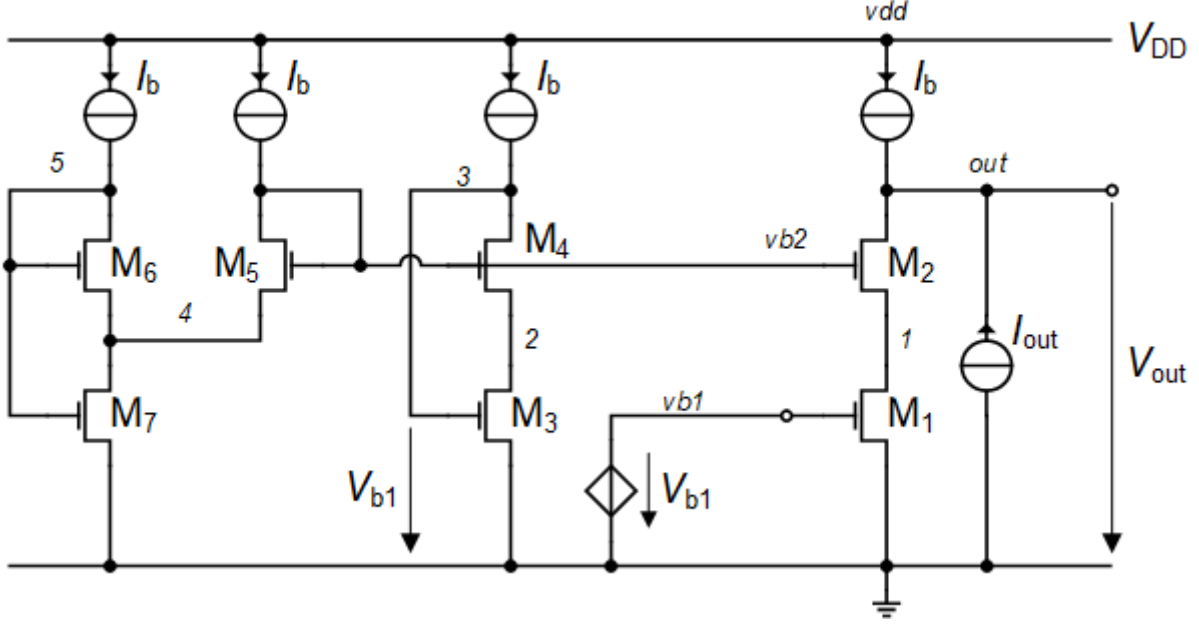


Figure 5.3: Schematic for simulating the output impedance.

theoretical expression

$$R_{out} = \frac{G_{ms2} + G_{ds1} + G_{ds2}}{G_{ds1}G_{ds2}} \cong \frac{G_{ms2}}{G_{ds1}G_{ds2}}. \quad (5.1)$$

The values of  $G_{ms2}$ ,  $G_{ds1}$  and  $G_{ds2}$  are extracted from PSP. We see a perfect match between the simulation and theoretical value of  $R_{out}$ .

 


Figure 5.4: Simulated output resistance compared to theoretical value.

The output resistance is increased by a factor

$$R_{out} \cdot G_{ds1} = \frac{G_{ms2} + G_{ds1} + G_{ds2}}{G_{ds2}} \cong \frac{G_{ms2}}{G_{ds2}} \quad (5.2)$$

which is about  $(G_{ms2} + G_{ds1} + G_{ds2})/G_{ds2} = 14.9$ .

This demonstrates that adding a cascode transistor significantly improves the output resistance at the cost of slightly less voltage headroom. It is particularly useful for this technology where the nMOS transistors have a very low output resistance.

## 5.4 Input-referred noise

We can now simulate the input-referred noise PSD and check whether the noise of the cascode transistor  $M_2$  is indeed much lower than the noise of the driver transistor  $M_1$ . To avoid the noise contribution of the biasing circuit, we set the bias voltages  $V_{b1}$  and  $V_{b2}$  with two voltage sources having the appropriate values extracted from the OP simulation, namely  $V_{b1} = 302 \text{ mV}$  and  $V_{b2} = 410 \text{ mV}$ . The input-referred noise PSD is plotted in Figure 5.5 and compared to the theoretical estimation. We see that the simulated white noise is reasonably close to the theoretical estimation, however the simulated flicker noise is smaller than the theoretical estimation. This comes from the fact that in PSP the gate-referred flicker noise is bias dependent which is not the case in the sEKV model.

The contributions of  $M_1$  and  $M_2$  to the input-referred white noise are shown in Figure 5.6. As expected, we can observe that the contribution of the cascode transistor  $M_2$  is more than 20 dB lower than that of  $M_1$ .

Figure 5.7 shows that the contribution of  $M_2$  to the input-referred flicker noise PSD. We can observe that the contribution of  $M_2$  is also about 20 dB lower than that of  $M_1$ .

The breakdown of the contributions of  $M_1$  and  $M_2$  to the total input-referred noise is summarized in Figure 5.8 which shows again that the noise contribution of  $M_2$  is more than 20 dB lower than that of  $M_1$ .

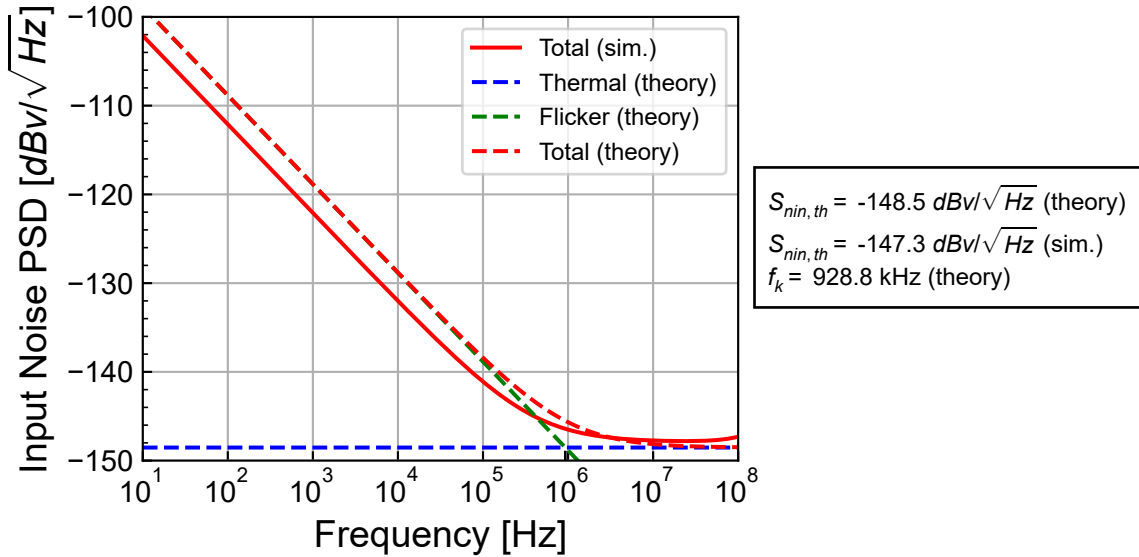


Figure 5.5: Simulated input-referred noise PSD compared to theoretical estimation.



 


Figure 5.6: Breakdown of the contributions to the simulated input-referred white noise PSD.

 


Figure 5.7: Breakdown of the contributions to the simulated input-referred flicker noise PSD.

 


Figure 5.8: Breakdown of the contributions to the simulated input-referred noise PSD.

## 6 Conclusion

In this notebook, we have first analyzed the cascode gain stage showing that the DC voltage gain is equivalent to a two-stage amplifier. We also have shown that the output resistance is increased by the voltage gain of the cascode transistor. In addition, the noise of the cascode transistor is much lower than that of the driver transistor and can usually be neglected. We then have designed the cascode gain stage for achieving a certain DC gain and gain-bandwidth product for a given load capacitance for the IHP SG13G2 130nm BiCMOS technology. A particular attention was brought to the design of the bias circuit to make sure that both transistors  $M_1$  and  $M_2$  are biased in weak inversion and in saturation. The circuit was then simulated with ngspice for the chosen IHP 130nm CMOS process taking advantage of the open source PDK. The simulation results are usually quite close to the values predicted by the theory. The simulations have also confirmed the main features of the cascode gain stage, namely a high voltage gain, high output resistance and low-noise. These features are achieved without increase of the current consumption (except the bias circuit which is needed anyway) thanks to the current reuse feature of the cascode stage.

# References

- [1] C. C. Enz and E. A. Vittoz, *Charge-Based MOS Transistor Modeling - The EKV Model for Low-Power and RF IC Design*, 1st ed. John Wiley, 2006.
- [2] C. Enz, F. Chicco, and A. Pezzotta, “Nanoscale MOSFET Modeling: Part 1: The Simplified EKV Model for the Design of Low-Power Analog Circuits,” *IEEE Solid-State Circuits Magazine*, vol. 9, no. 3, pp. 26–35, 2017.
- [3] C. Enz, F. Chicco, and A. Pezzotta, “Nanoscale MOSFET Modeling: Part 2: Using the Inversion Coefficient as the Primary Design Parameter,” *IEEE Solid-State Circuits Magazine*, vol. 9, no. 4, pp. 73–81, 2017.
- [4] IHP, “IHP SG13G2 Open Source PDK.” <https://github.com/IHP-GmbH/IHP-Open-PDK>, 2025.
- [5] IHP, “IHP SG13G2 DC CV NMOS LV Documentation (Rev. 1.2).” [ihp-sg13g2/libs.doc/meas/MOS/doc/report\\_nmos\\_lv.pdf](ihp-sg13g2/libs.doc/meas/MOS/doc/report_nmos_lv.pdf), 2023.
- [6] G.D.J. Smit, A.J. Scholten, D.B.M. Klaassen, O. Rozeau, S. Martinie, T. Poiroux and J.C. Barbé, “PSP 103.6 - The PSP model is a joint development of CEA-Leti and NXP Semiconductors.” [https://www.cea.fr/cea-tech/leti/pspsupport/Documents/psp103p6\\_summary.pdf](https://www.cea.fr/cea-tech/leti/pspsupport/Documents/psp103p6_summary.pdf), 2017.
- [7] SemiMod GmbH, “Open VAF.” <https://openvaf.semimod.de/docs/getting-started/introduction/>, 2025.
- [8] Dietmar Warning, “Verilog-A Models for Circuit Simulation.” <https://github.com/dwarning/VA-Models>, 2024.
- [9] Agilent Technologies, “IC-CAP 2008, Nonlinear Device Models - Volume 1.” [https://people.ece.ubc.ca/robertor/Links\\_files/Files/ICCAP-2008-doc/pdf/icmdl.pdf](https://people.ece.ubc.ca/robertor/Links_files/Files/ICCAP-2008-doc/pdf/icmdl.pdf), 2008.